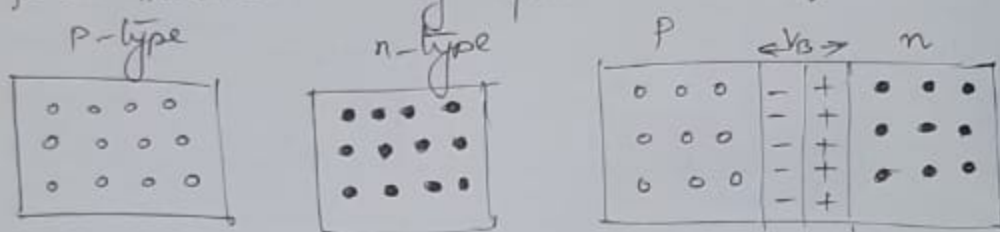





## PN Junction:

When a p-type semiconductor is suitably joined to n-type semiconductor the contact surface is called pn junction. ①

Most of the semiconductors have more than one or more pn junction. PN junction is fabricated by special techniques.





When a pn junction is formulated suitably, there is a tendency for the free electrons from n-side to diffuse over the p-side of the junction, and holes from p-side to n-side. Both the regions are initially electrically neutral, a positive charge is built on the n-side and negative charge on the p-side of the junction. This situation soon prevents further diffusion. It is because now positive charge on n-side repels holes to cross from p-type to n-type and negative charge on the p-side repels free electrons to

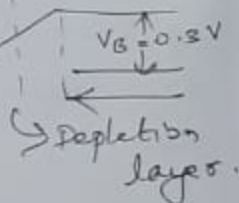



ent from n-type to p-type. This a barrier<sup>(2)</sup> is set up against further movement of charge carriers i.e., holes and free electrons. This is called potential barrier. potential barrier is of the order of 0.1 to 0.7 V.

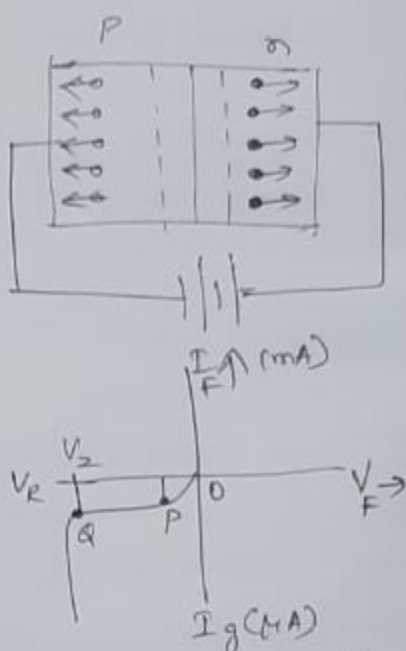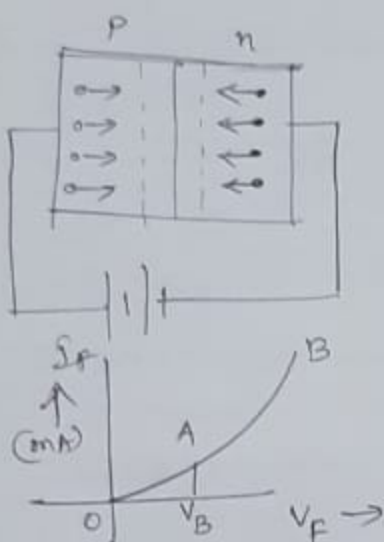V-I characteristics of pn junction diode:-



Forward bias:-

To apply forward bias connect positive terminal of the battery to p-type and negative terminal to n-type. The applied forward potential establishes an electric field which acts against the field due to potential barrier. As potential barrier is very small (0.1 to 0.7 V), therefore



a small forward voltage is sufficient to <sup>③</sup> completely eliminate the potential barrier. Once the pot. barrier is eliminated by the forward bias, junction resistance becomes almost zero, and current flows in the circuit.

① The potential barrier is reduced and at some forward bias it is eliminated.

(0.3 to 0.7 V)

② The junction offers low resistance to current flow.

③ Current flows in the circuit depends on applied forward voltage.

$V_F - I_F$  curve: The current increases very slowly and the curve is non-linear. It is because the external applied voltage is used in overcoming the potential barrier. However once the external voltage exceeds the potential barrier voltage the pn junction becomes like an ordinary conductor. The curve is almost linear.

Reverse biasing:

When an external d.c voltage applied to a pn junction, is in such a direction that potential barrier is increased, it is called reverse biasing.





To apply reverse bias, connect negative <sup>(4)</sup> terminal of battery to p-type and positive terminal to n-type. Graph shows <sup>clearly</sup> that reverse voltage establishes an electric field which acts in the same direction as the field due to potential barrier. The increased potential barrier prevents the flow of charge carriers across the junction. Thus a high resistance path is established for the entire circuit and hence current does not flow.

- ① Potential barrier is increased.
- ② The junction offers very high resistance to current flow.
- ③ No current flows in the circuit due to high resistance path.


$V_R - I_R$  curve: A small current in  $\mu A$  flows in the circuit under reverse bias. This is called as reverse current due to minority carriers. Electrons in p-type and holes in n-type are called minority carriers. Hence very small current flows in reverse direction called as leakage current and as the reverse voltage



is increased breakdown ( $V_Z$ ) occurs, or reached breakdown voltage ( $V_Z$ ). It breaks the covalent bonds, creating a large number of minority carriers. Consequently a sudden rise in reverse current and sudden fall of resistance of barrier region. This may permanently damage the junction due to excess heat.





Breakdown voltage: It is the minimum reverse voltage at which the pn junction breaks down with sudden rise in reverse current. When high reverse voltage is applied electrons acquire high velocity, we get an avalanche of free electrons. Therefore pn junction conducts large reverse current.

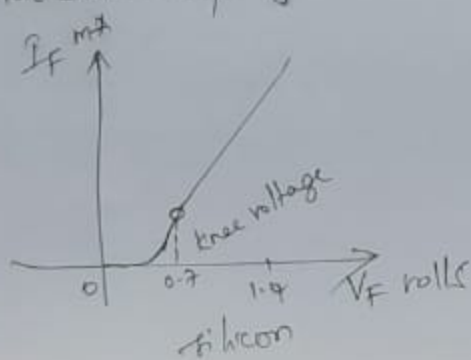Knee voltage: It is the forward voltage at which the current through the junction starts to increase rapidly.



When a diode is forward biased, it conducts  $\textcircled{b}$ , current slowly until we overcome the potential barrier. For Silicon potential barrier is  $0.7\text{ eV}$ . Once the applied force voltage exceeds the knee voltage, the current starts increasing rapidly. The applied voltage should exceed knee voltage.

### Half wave rectifier:-

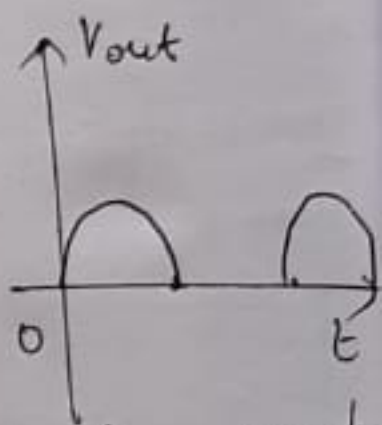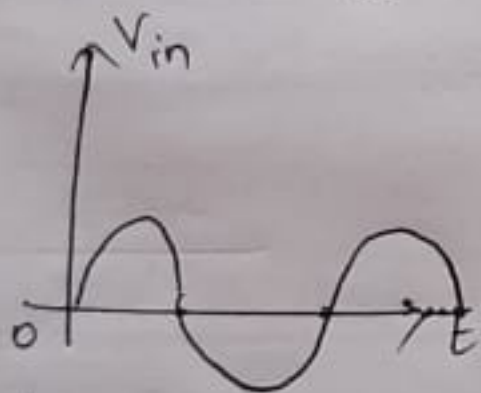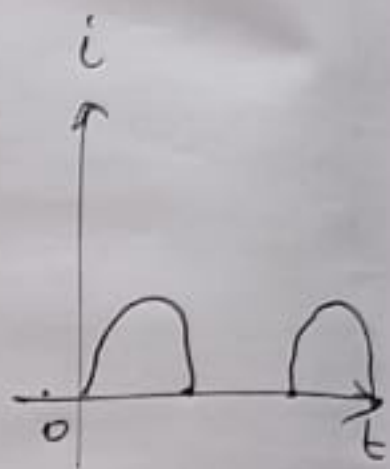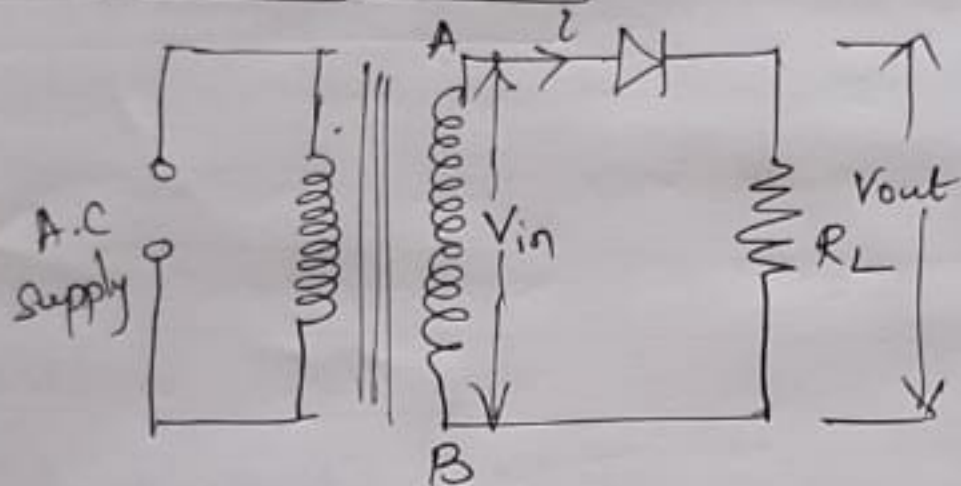

### Rectifiers:

There are many appliances where d.c supply is needed. When such a d.c supply is needed, the main a.c supply is rectified by using crystal diodes.

- 1) Half wave rectifier
- 2) Full wave rectifier





Working! The a.c voltage across the <sup>(2)</sup> secondary winding AB changes polarity after every half-cycle. During +ve half-cycle of input a.c voltage, end A becomes positive w.r.t end B. This makes the diode forward biased and hence it conducts current.

During -ve half cycle end A is negative w.r.t end B. Under this condition the diode is reverse biased and it conducts no current.

∴ Current flows through the diode during positive half cycle of input a.c voltage, only and blocked during -ve half cycle. Current flows through the load  $R_L$  always in the same direction. Hence d.c output is obtained across  $R_L$ . It may be noted that output across the load is pulsating d.c. These are smoothened with the help of filter circuits.



O/p frequency: O/p frequency is the same as i/p frequency. In both the cases the waveform completes one cycle every  $360^\circ$  or repeats same pattern every  $360^\circ$ .

$$f_{out} = f_{in}$$

Disadvantages:

- ① The output is a pulsating current,  $\therefore$  an elaborate filtering is required to produce steady current.
- ② The a.c supply delivers only half the time.  $\therefore$  O/p is very low.

Efficiency:  $\eta = \frac{\text{d.c power o/p}}{\text{i/p a.c. power}}$

$$V_m \sin \theta = V_m \sin \theta - \text{across } AB$$

$r_f$  and  $R_L$  - diode and load resistances

$$\therefore i = \frac{V}{r_f + R_L} = \frac{V_m \sin \theta}{r_f + R_L}$$

When  $\theta = 90^\circ$  d.c current is maximum

$$\therefore I_m = \frac{V_m}{r_f + R_L}$$





d.c. power: Since it is pulsating current, <sup>(4)</sup>  
In order to find power, average current has to be found out.

Average current  $I_{dc} = \frac{I_m}{\pi}$

$$I_m = \frac{V_m}{r_f + R_L}$$

Average voltage =  $\frac{V_m}{\pi}$

D.c power  $P_{dc} = I_{dc}^2 R_L$   
 $= \left( \frac{I_m}{\pi} \right)^2 R_L$

a.c power:  $P_{ac} = I_{rms}^2 (r_f + R_L)$

for a half-wave rectified wave  $I_{rms} = \frac{I_m}{2}$

$$\therefore P_{ac} = \left( \frac{I_m}{2} \right)^2 (r_f + R_L)$$

$$\therefore \eta = \frac{P_{dc}}{P_{ac}} = \frac{\left( \frac{I_m}{\pi} \right)^2 R_L}{\left( \frac{I_m}{2} \right)^2 \times (r_f + R_L)}$$



(5)

$$= \frac{0.406 R_L}{r_f + R_L} = \frac{0.406}{1 + \frac{r_f}{R_L}}$$

$\eta$  is maximum when  $r_f$  is negligible when compared to  $R_L$

Max. rectifier efficiency = 40.6%

Peak Inverse Voltage: When the diode is reverse biased, the load current is zero. so that there is no voltage across load  $R_L$ .  $\therefore$  entire  $V_m$  will appear across diode as reverse bias  $PIV = V_m$  — Half wave rectifier.

Problem: A crystal diode having  $r_f = 20 \Omega$  is used for half-wave rectification. If the applied voltage is  $V = 50 \sin \omega t$  and load resistance  $R_L = 800 \Omega$  find (i)  $I_m$ ,  $I_{dc}$ ,  $I_{rms}$   
(ii) a.c. power input, d.c power output  
(iii) d.c. o/p voltage (iv)  $\eta$

Maximum voltage = 50 V.



$$I_m = \frac{V_m}{r_f + R_L} = \frac{50}{20 + 800} = 0.061 \text{ A} = 61 \text{ mA} \quad (6)$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{61}{\pi} = 19.4 \text{ mA}$$

$$I_{rms} = \frac{I_m}{2} = \frac{61}{2} = 30.5 \text{ mA}$$

$$P_{ac} = I_{rms}^2 (r_f + R_L)$$

$$= (30.5 \times 10^{-3})^2 \times (20 + 800) = 0.763 \text{ W}$$

$$P_{dc} = I_{dc}^2 \times R_L = (19.4 \times 10^{-3})^2 \times 800 = 0.301 \text{ W}$$

$$\text{D.C. o/p voltage} = I_{dc} \times R_L = 19.4 \text{ mA} \times 800 \Omega = 15.52 \text{ V}$$



also

$$\text{D.C. o/p voltage} = \frac{V_m}{\pi} = \frac{50}{\pi} = 15.52 \text{ V}$$

$$\eta = \frac{0.301}{0.763} \times 100 = 39.5\%$$



D.C. power,  $P_{dc} = I_{dc} R_L = (I_m/\pi) R_L$

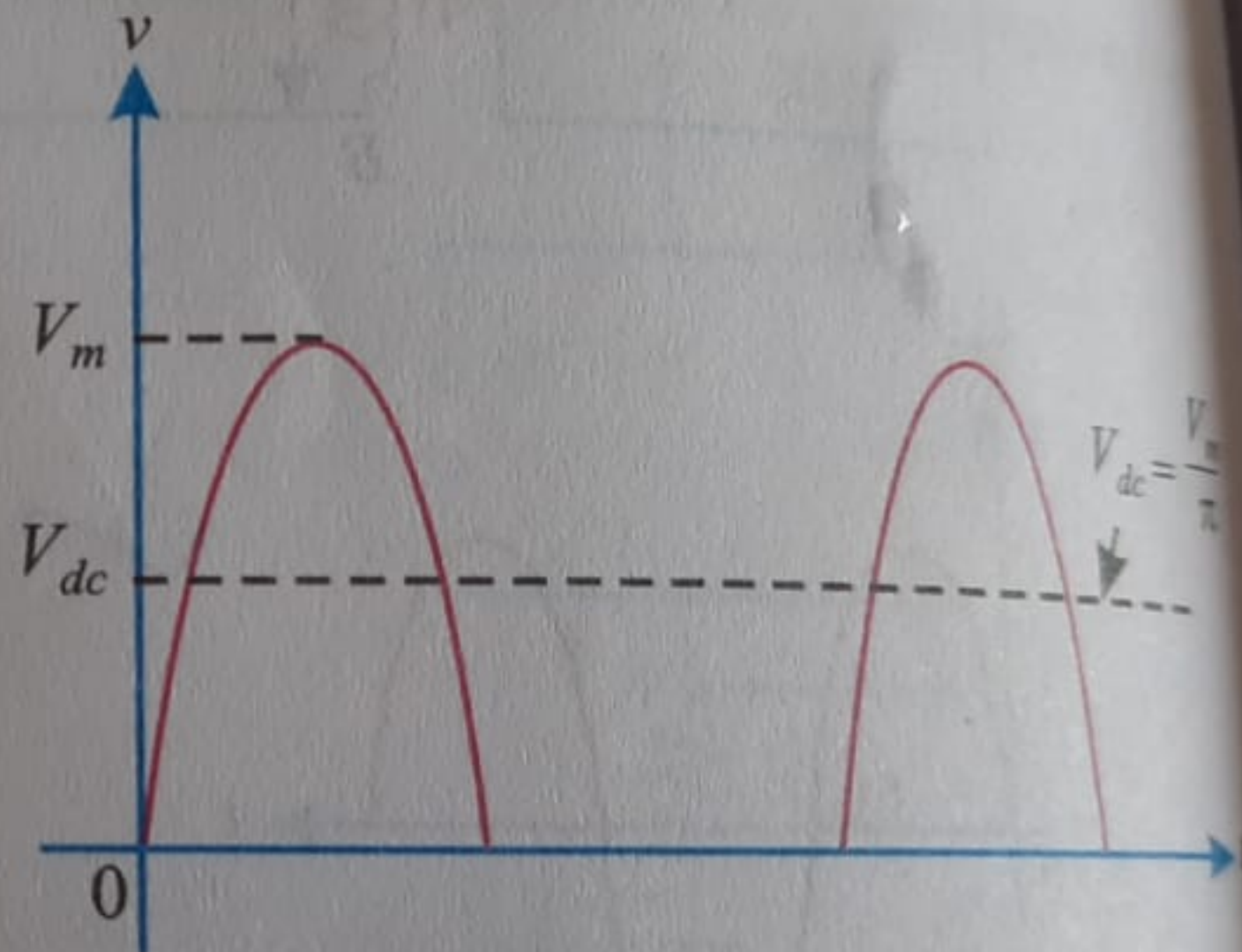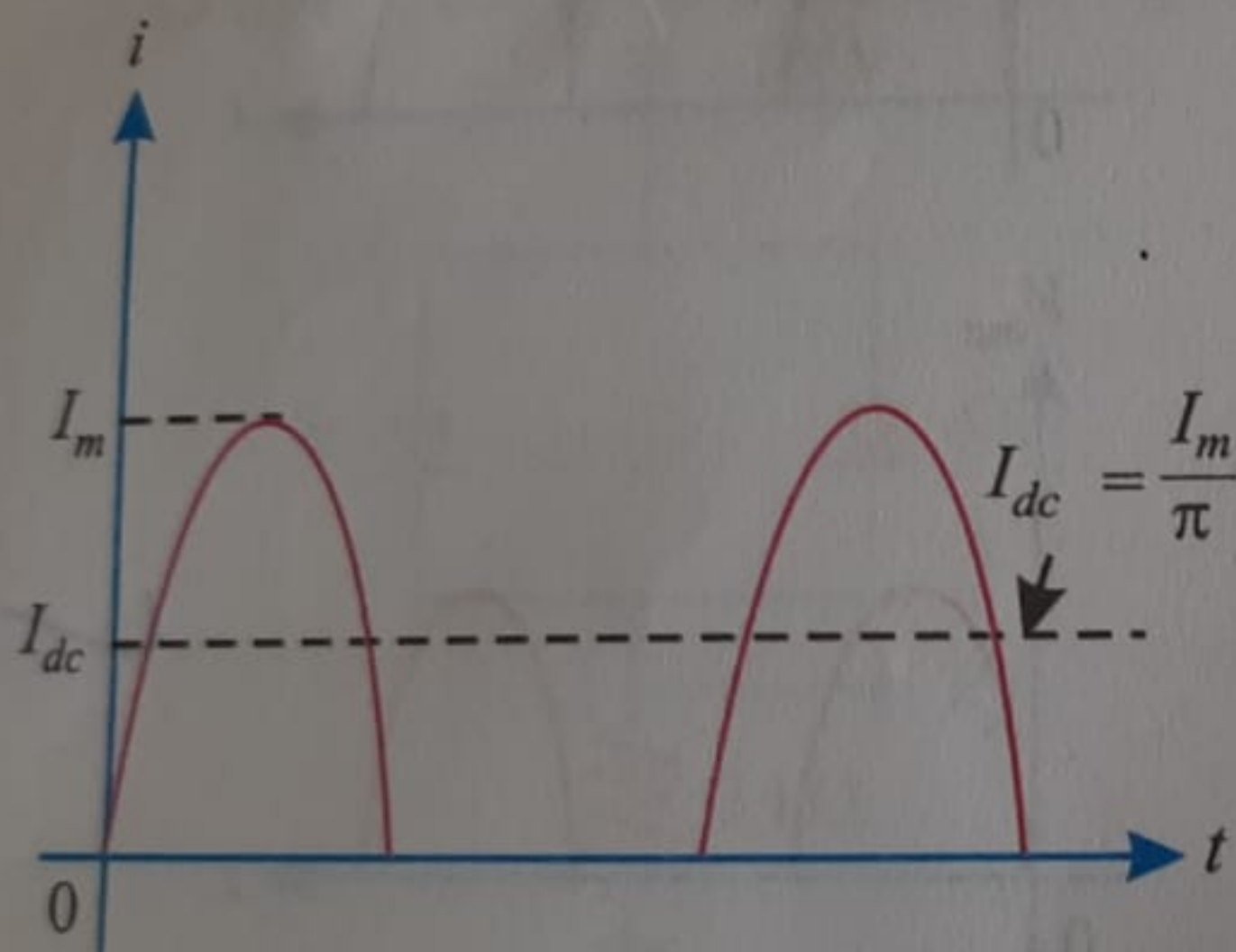

**Fig. 26.14**

$$P_{ac} = I_{r.m.s.}^2 (r_f + R_L)$$

ac power input  
Samsung Triple Camera  
Galaxy A30s

For a half-wave rectified wave,  $I_{r.m.s.} = I_m/\sqrt{2}$ .

problem: 2 A half wave rectifier is used to supply 50V d.c to a resistive load of  $800\ \Omega$ . The diode has a resistance of  $25\ \Omega$ . Calculate the maximum value of a.c. voltage required.






## Full - wave Rectifier:

①

In full wave rectifier, current flows through the load in the same direction for both half cycles of i/p a.c voltage.

## Centre - Tap Full - wave Rectifier

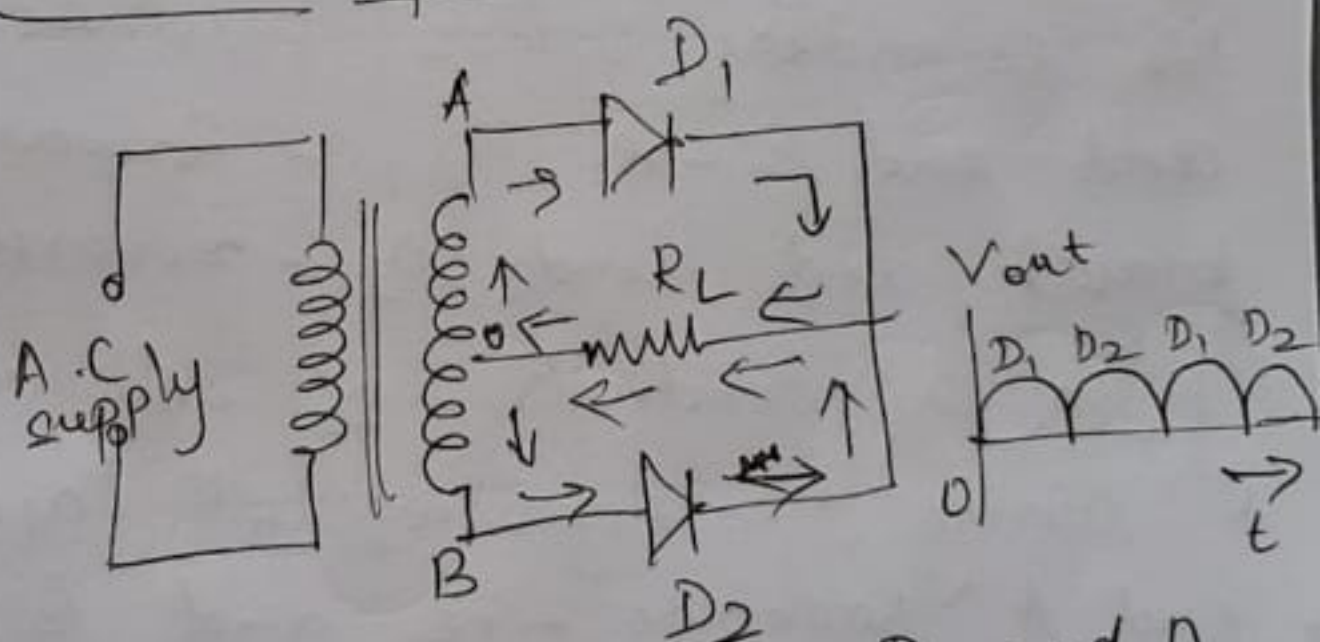

There are two diodes  $D_1$  and  $D_2$ . A centre tapped secondary winding AB is used with diodes connected so that each uses half cycle of input a.c voltage.



Samsung Triple Camera

Galaxy A30s



(2)  
Diode  $D_1$  utilizes the a.c voltage appearing across the upper half of secondary windings while  $D_2$  uses lower half.

operation: (i) During the half-cycle of secondary voltage, the end A of the secondary winding becomes +ve and end B -ve.  $D_1$  - forward biased and diode  $D_2$  - reverse biased.

When  $D_1$  conducts  $D_2$  will not.

(ii) During the negative half-cycle end A becomes -ve and B +ve.

$\therefore D_2$  conducts while  $D_1$  does not.

Dis Advantages: (i) It is difficult to



locate the centre tap on the secondary windings.

(ii) o/p is small utilizes only  $\frac{1}{2}$  of voltage

(iii) Diodes should have high PIV




## Full wave Bridge Rectifier

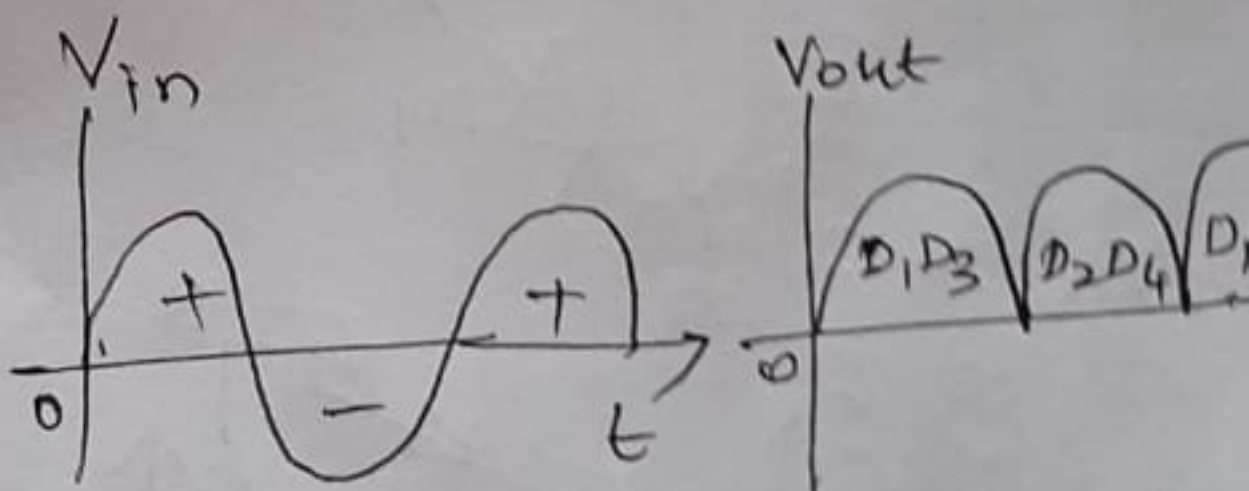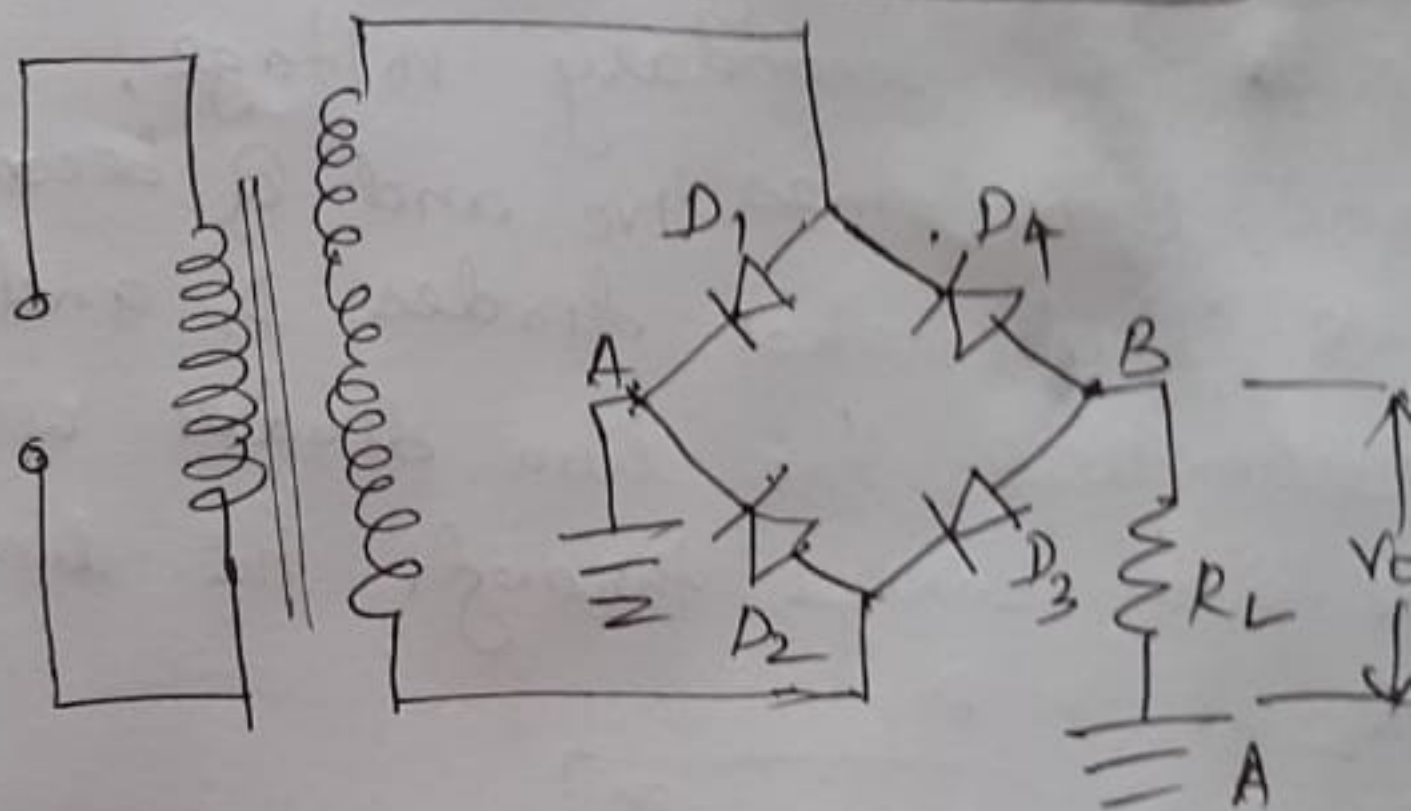

There are 4 diodes  $D_1, D_2$  and  $D_4$  connected to form bridge



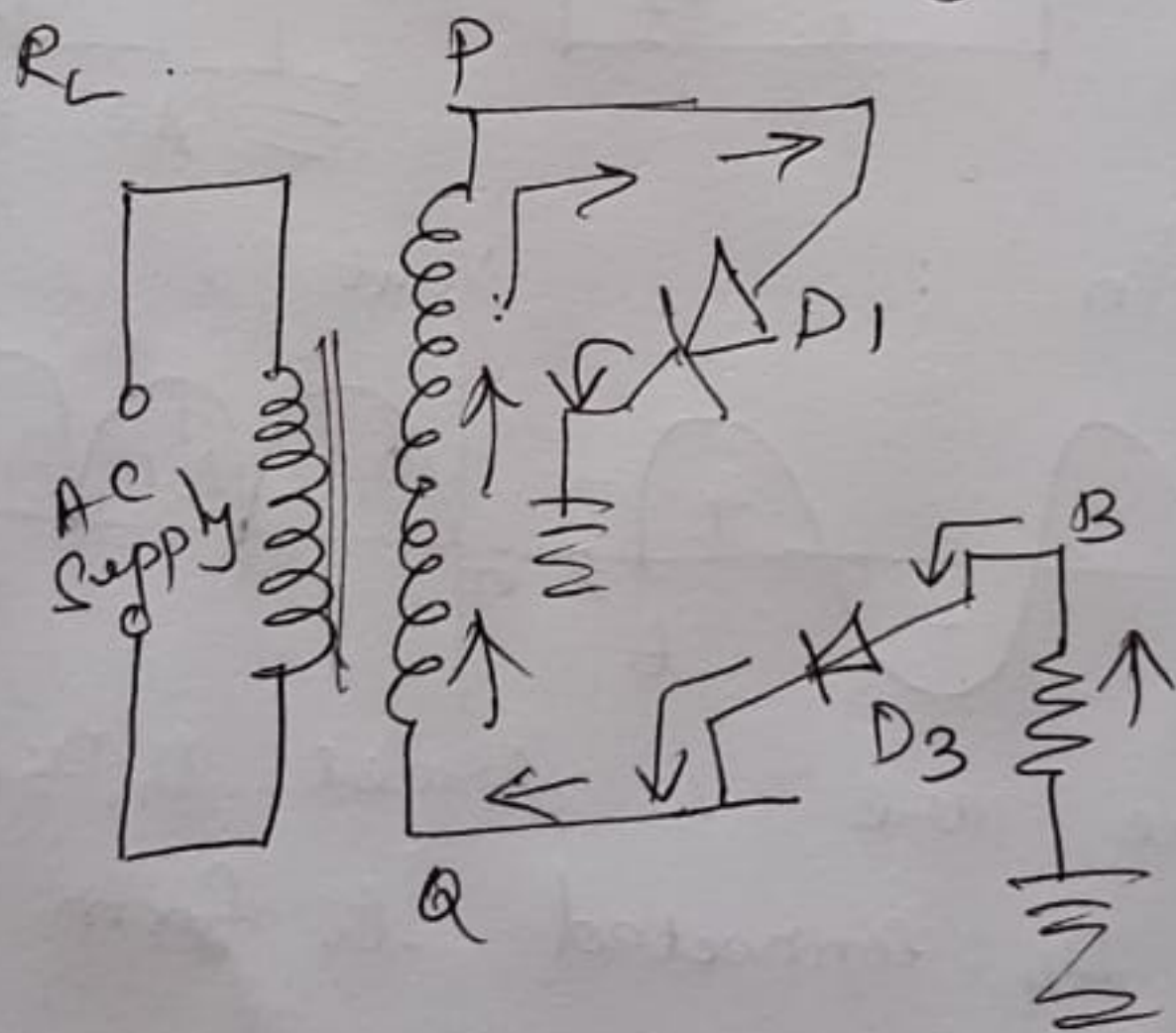
operation: During positive half cycle of secondary voltage, end P becomes +ve and Q becomes -ve. This makes diodes  $D_1$  and  $D_3$  conduct. The two diodes will be in series through the load





During -ve half cycle end P becomes negative and Q +ve. This makes diodes  $D_2$  and  $D_4$  forward biased while diodes  $D_1$  and  $D_3$  are reverse biased.  $\therefore$

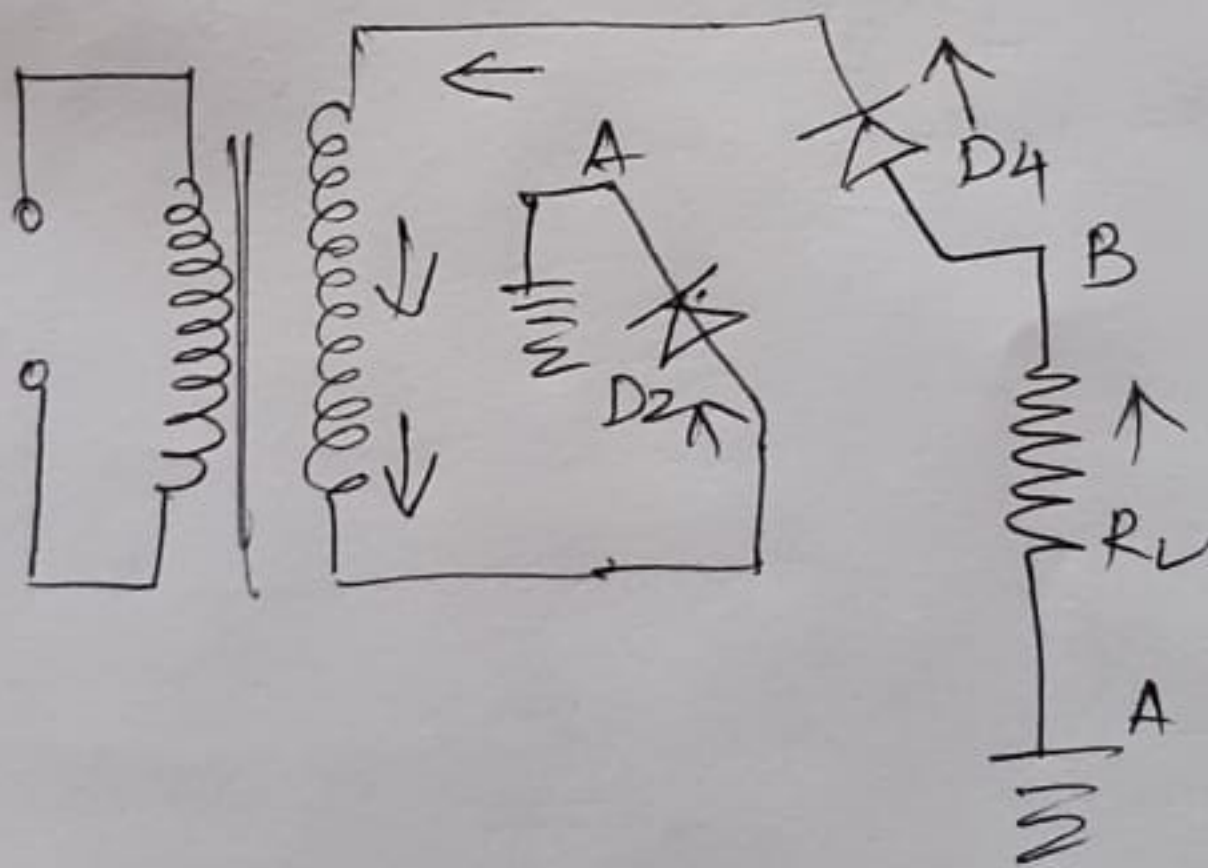$D_2$  and  $D_4$  will conduct. D.C output is obtained across the load  $R_L$ .



### Advantages:

- (i) No need for centre tap
- (ii)  $\phi/p$  is twice that of centre tap circuit
- (iii) For the same d.c output voltage PIV of bridge circuit is half that of the centre tap circuit.



half (4)

$$q: V = V_m \sin \theta \quad (7)$$

$r_f, R_L$  - diode and load resistance. The rectifier will conduct current through the load in the same direction for both half-cycles of input ac voltage.

$$i = \frac{V}{r_f + R_L} = \frac{V_m \sin \theta}{r_f + R_L}$$

$i$  is maximum when  $\theta = 90^\circ$

$$I_m = \frac{V_m}{r_f + R_L}$$

d.c power output

$$I_{dc} = \frac{2 I_m}{\pi}$$

$$I_m = \frac{V_m}{r_f + R_L}$$

$$V_m = \frac{2 V_m}{\pi}, \quad P_{dc} = I_{dc}^2 \times R_L \\ = \left( \frac{2 I_m}{\pi} \right)^2 \times R_L$$





a.c power i/p

(8)

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}, \quad P_{ac} = I_{\text{rms}}^2 (r_f + R_L)$$

$$= \left( \frac{I_m}{\sqrt{2}} \right)^2 \times (r_f + R_L)$$

$$\text{Rectifier } \eta = \frac{P_{dc}}{P_{ac}}$$

$$= \frac{\left( \frac{2I_m}{\pi} \right)^2 \times R_L}{\left( \frac{I_m}{\sqrt{2}} \right)^2 (r_f + R_L)} = \frac{0.812 R_L}{r_f + R_L}$$

$$= \frac{0.812}{1 + \left( \frac{r_f}{R_L} \right)}$$

If  $r_f$  is negligible  $\eta$  is maximum  
= 81%.

Twice that of half-wave rectifier.



## Electromagnetism :


①

### Electromagnetic Induction:-

Whenever an electric current flows through a conductor, a magnetic field is immediately brought into existence in the space surrounding the conductor.

It can be noted that when electrons are in motion, they produce a magnetic field. The converse of this is true.

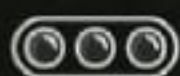
When a magnetic field embracing a conductor moves relative to the conductor, it produces flow of electrons in the conductor. When current is induced in any conductor which





is cut across a magnetic flux <sup>(2)</sup>  
is known as electromagnetic  
induction.

### Production of EMF :

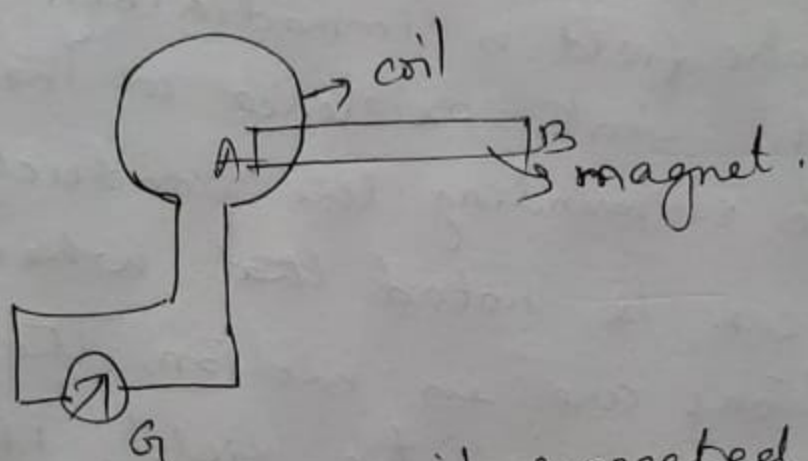

Consider a coil connected to a galvanometer; AB is a magnet, when the magnet is brought near the coil and moved through the coil we can see the galvanometer is deflected. When the magnet is stationary there is no generation of EMF. Only when the flux





lines linked with coil is (3).  
disturbed there is generation  
of emf.

When the magnet AB is  
kept stationary and the coil is  
moved suddenly towards <sup>or away</sup> the  
coil current is generated.

Faraday's law:

First law: Whenever the magnetic  
flux linked with a circuit  
changes, an emf is always induced  
in it.

Second law:

The magnitude of the induced  
emf is equal to the rate of  
change of flux-linkages.



If there are  $N$  number of ④ coils, and flux through it changes from an initial value of  $\phi_1$  to the final value  $\phi_2$  webers in  $t$  seconds, then

$$\text{induced emf} = e = \frac{N\phi_2 - N\phi_1}{t} \text{ weber}$$

$$\text{or } e = N \left( \frac{\phi_2 - \phi_1}{t} \right) \text{ volt.}$$

$$e = \frac{d}{dt} (N\phi) = -N \frac{d\phi}{dt} \text{ volt}$$

-ve sign indicates that induced emf is opposite to the direction of magnetic effect.

According to Fleming's Right hand rule, when fore finger, middle finger and thumb are kept



$\perp$  to each other, Thumb — (5)  
Points the direction of the conductor  
Fore finger — direction of the  
magnetic field  
Middle finger direction of the  
emf.


Lenz's law :

Electromagnetically induced  
current always flows in such  
direction that the action of the  
magnetic field set up by it tends  
to oppose the very cause which  
produces it.

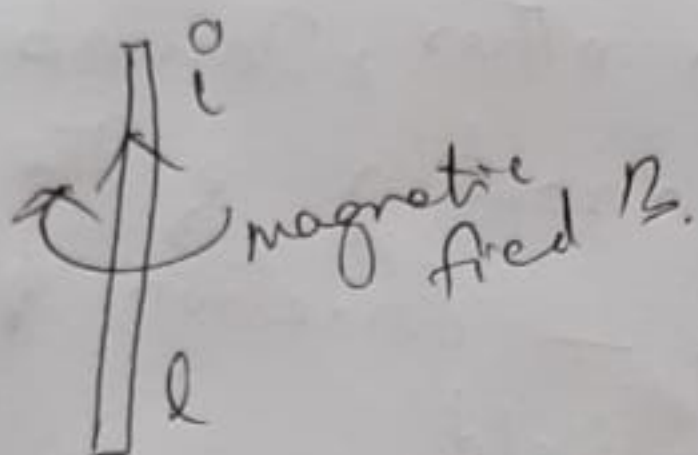When a wire carries current  
of length  $l$  and current  $i$ ,  
A magnetic field developed  
perpendicular to the wire.








(6)

Dynamically induced emf:

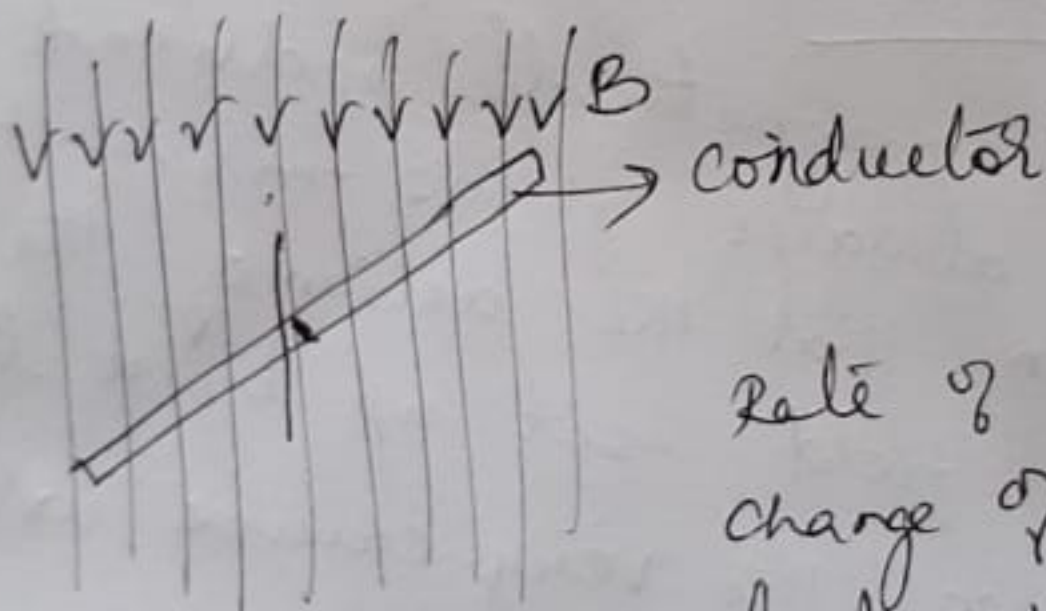


Rate of  
change of flux  
linkages  $= Bl \frac{dx}{dt}$

$= Blv \sin \theta$


$\theta$  - with direction of flux.

$$e = B l v \text{ volts}$$

$$(\because dx/dt = v)$$

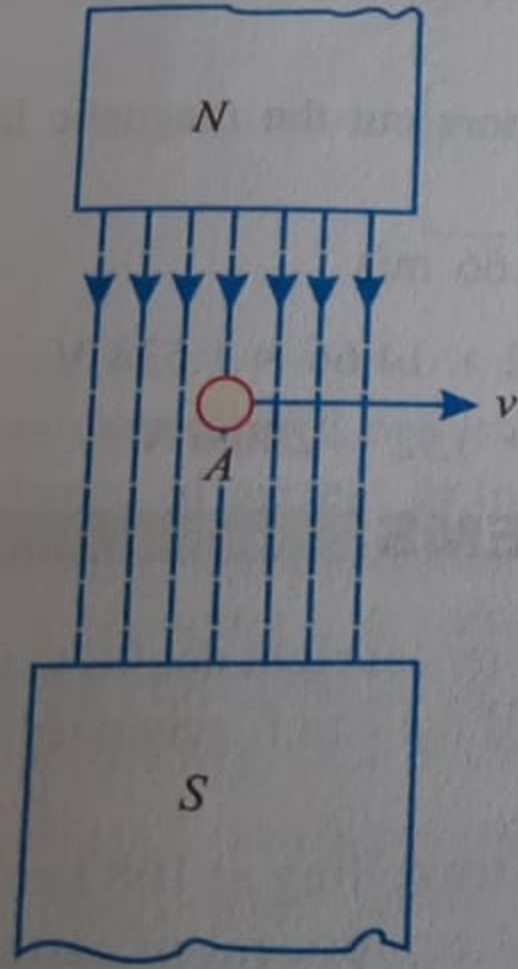

(i)

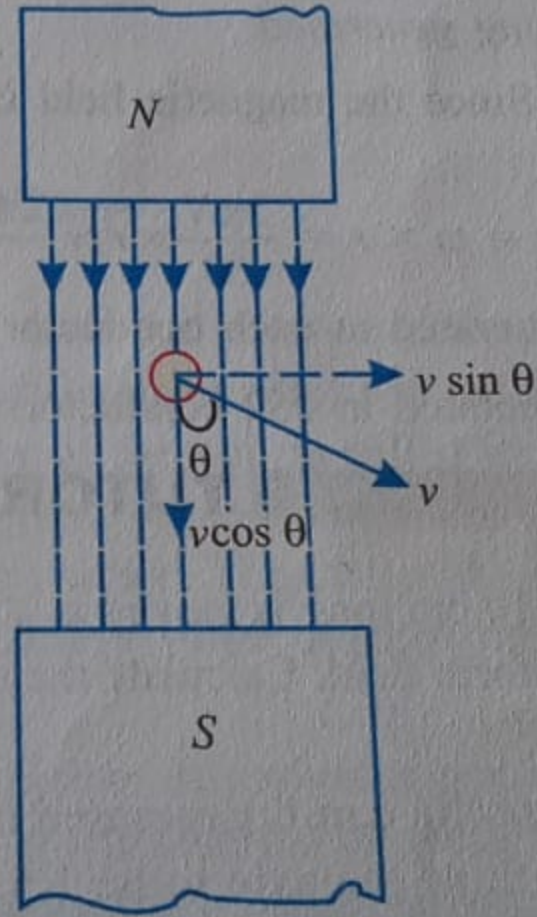

(ii)



## Zener Diode:

①


- ① Already we know that when reverse bias on a crystal diode is increased a critical voltage called breakdown voltage is reached where the reverse current increases rapidly or sharply at a high value.
- ② The breakdown region is the knee of the reverse characteristics as shown in diagram (i)
- ③ The breakdown voltage some times called as zener voltage and the sudden increase in current is known as zener current.
- ④ The breakdown or zener voltage depends on the amount of doping. If the diode is heavily doped, depletion layer will be very thin, the junction will occur at low reverse voltage.
- ⑤ If the diode is lightly doped, has a higher breakdown voltage
- ⑥ When an ordinary diode is properly doped so that it has a sharp breakdown voltage. It is called as zener diode.



Samsung Triple Camera

Galaxy A30s



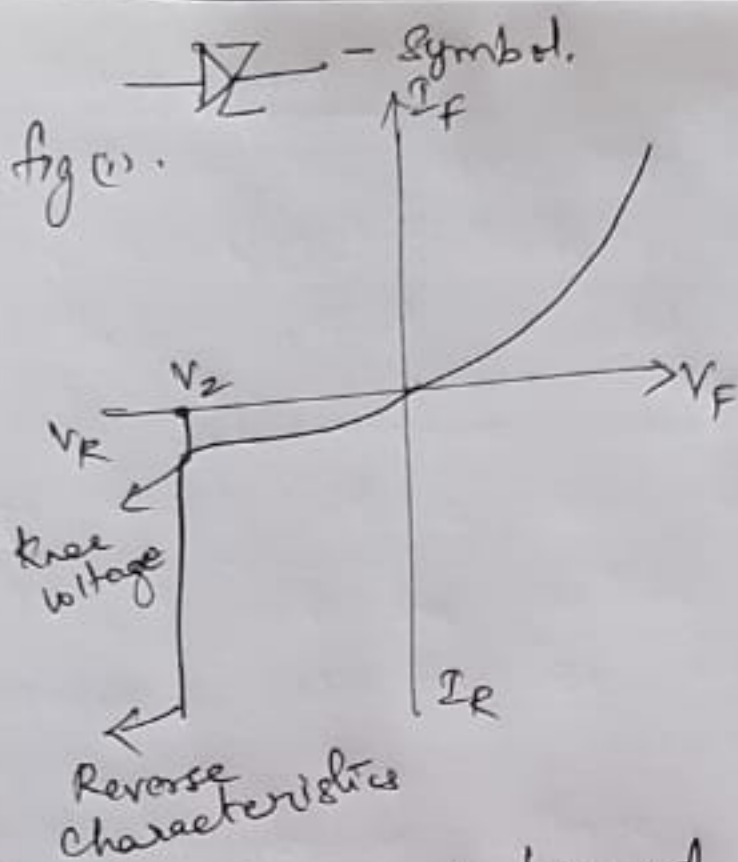

① A zener diode is like an ordinary diode except that it is properly doped so that it has a sharp breakdown voltage.



② It is always reverse biased.

③ Sharp breakdown voltage  $V_Z$

④ When forward biased behaves as an ordinary diode.


⑤ Zener diode will not be immediately burnt since it has a breakdown region which limits diode current. Unless the external applied current exceeds burn out value the diode will not be burnt.

## Zener Diode's Equivalent circuit:

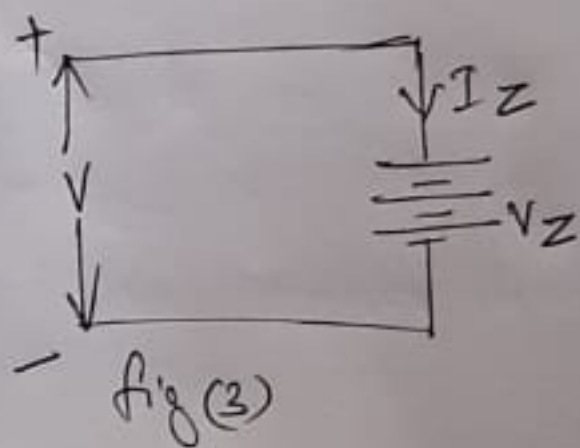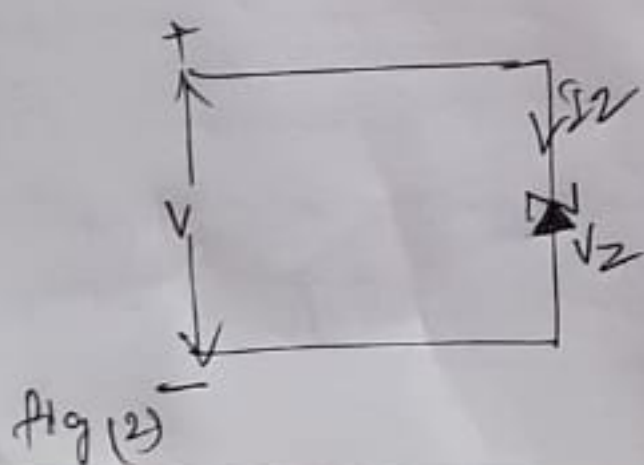

① ON state: When reverse voltage across a Zener diode is equal to or more than breakdown voltage  $V_Z$ , the current increases very sharply. Voltage across the Zener diode is constant  $V_Z$  even though the current through it changes. Now diode is in the ON state.


② OFF state:

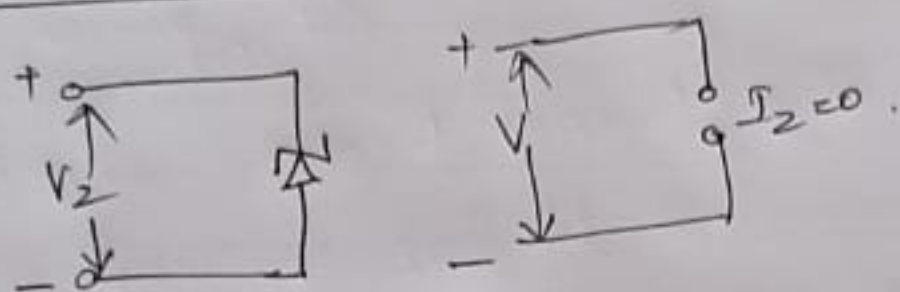

When the reverse voltage across the Zener diode is less than  $V_Z$  but greater than 0V, the Zener diode is in the OFF state. Now it can be represented as open-circuit Zener diode as a voltage stabilizer.

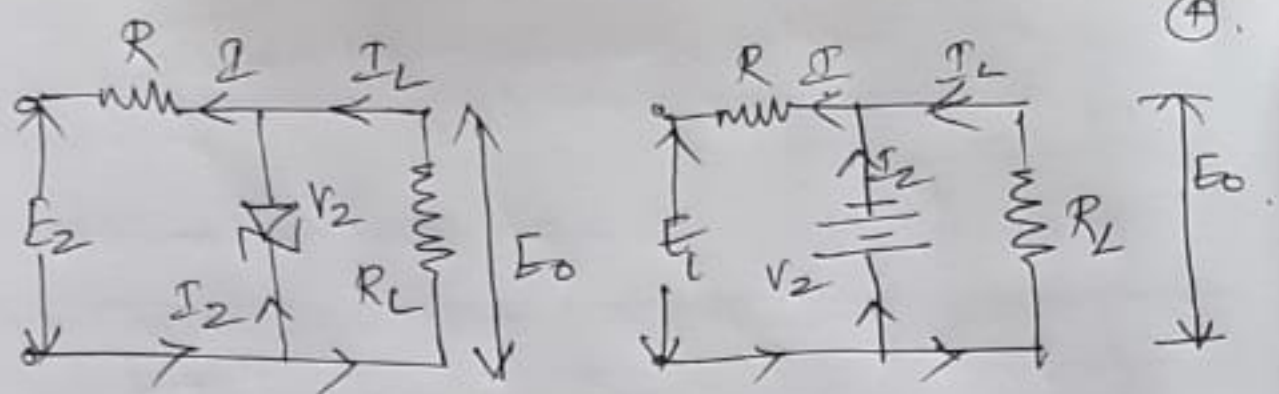A Zener diode can be used as a voltage regulator to provide a constant voltage from a source whose voltage may vary.





- ① The Zener diode of Zener voltage  $V_Z$  is reverse connected across the load  $R_L$  across which the constant output is desired. The series resistance  $R$  absorbs the output voltage fluctuations so as to maintain constant voltage across the load.
- ② Zener diode will maintain a constant voltage ( $V_Z = E_0$ ) across the load so as long as the input voltage does not fall below  $V_Z$ .
- ③ Suppose the input voltage increases; since Zener is in the breakdown region the Zener diode is equivalent to a battery  $V_Z$ . It is clear that the output voltage remains constant at  $V_Z$ . The excess voltage is dropped across the series resistance  $R$ .



⑤ This will cause an increase in the value of total current  $I$ . The zener will conduct the increase of current in  $I$  while the load current remains constant. The o/p voltage  $E_o$  remains constant irrespective of change in input voltage  $E_i$ .

④ If  $R_L \downarrow$  - will cause an increase in load current. The extra current cannot come from the source because drop in  $R$  will not change as the zener is within its regulating range. The additional load current will come from a  $\downarrow$  of zener current  $I_z$ ; o/p voltage is constant.



Voltage drop across  $R = E_i - E_o$

Current through  $R$ ,  $I = I_z + I_L$

$$R = \frac{E_i - E_o}{I_z + I_L} = \frac{V}{I}$$



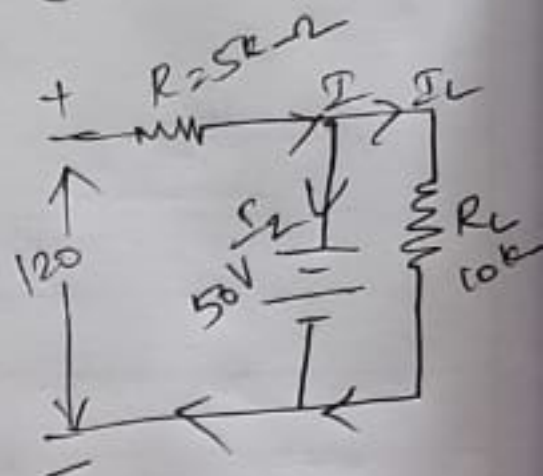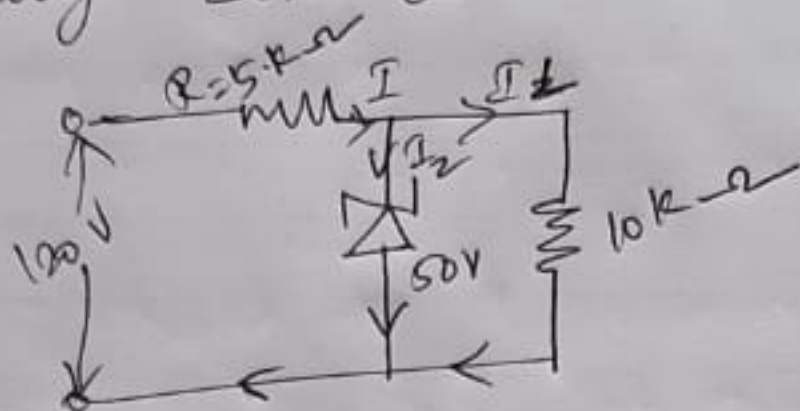Problem:- Find (i) the o/p voltage (ii) voltage drop across series resistance (iii) the current through zener diode. (6)



If we remove zener diode,  $V$  across open circuit  $V = \frac{R_L E_i}{R + R_L} = \frac{10 \times 120}{5 + 10} = 80V$

Since voltage across zener diode is greater than  $V_Z = 50V$  the diode is in the ON state.

Output voltage,  $V_Z = 50V$


Voltage drop across  $R = \text{Input voltage} - V_Z$   
 $= 120 - 50 = 70V$

Load current  $I_L = \frac{V_Z}{R_L} = \frac{50V}{10k\Omega} = 5mA$

current through  $R, I = \frac{70V}{5k\Omega} = 14mA$

$$I = I_L + I_Z$$

$$I_Z = I - I_L = 14 - 5 = 9mA$$

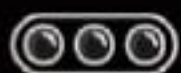




## Statically Induced emf:

(1)

When the conductor is stationary and field is moving or changing, the emf induced in the conductor is called statically induced emf.

- 1) Self induced emf
- 2) Mutually induced emf.

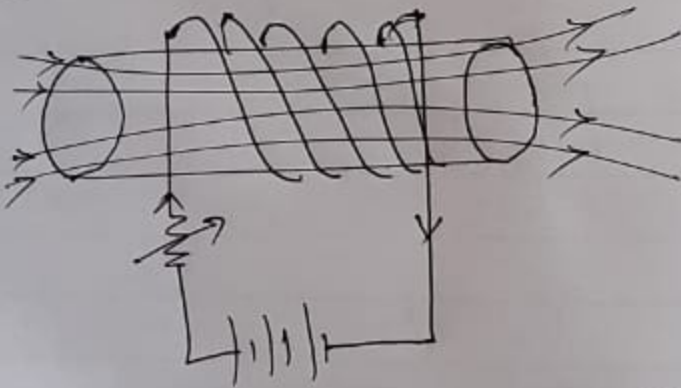1) Self induced emf: The emf induced in a coil due to the change of its own magnetic flux with it is called self-induced emf.



When a coil is carrying current a magnetic field is established through the coil. If the current in the coil changes,



Samsung Triple Camera  
Galaxy A30s




Then magnetic flux linking the coil also changes.  
Hence by Faraday's laws, an emf will be induced in the coil.

$$\text{Self induced emf} = -N \frac{d\phi}{dt}$$

Lenz's law: The direction of induced emf is always such as to oppose the cause responsible for inducing the emf namely change in current and hence field in the coil.
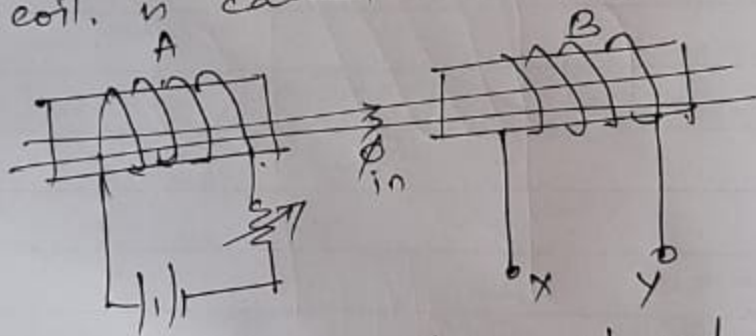
## 2) Mutually induced emf:

The emf induced in a coil due to the changing current in the neighbouring coil, is called mutually induced emf.



Two coils A and B placed adjacent to each other. Magnetic flux produced by the coil A link with B. The flux common to both A and B is called



mutual flux ( $\phi_m$ ). If the current<sup>(2)</sup> in the coil is varied the actual flux also varies and hence emf is induced in both the coils. Emf induced in coil A is called self inductance and coil B is called as mutual inductance.

$$e_m = N_B d\phi_m / dt.$$

$N_B$  - no of turns in coil B.

$\frac{d\phi_m}{dt}$  = rate of change of flux in both the coils.

① The mutually induced emf in coil B persists so long as the current in the coil A is changing. If the current becomes steady the mutual flux becomes steady and mutually induced emf reduces to zero.

② The property of two neighbouring coils to induced voltage in one coil due to the change of current in the other is called mutual inductance.



Expression for self inductance:

(4)

$$e = N \frac{d\phi}{dt} = \frac{d}{dt} (N\phi)$$

$$e = \frac{d}{dt} (N\phi) \propto \frac{dI}{dt}$$

$$e = \text{constant} \times \frac{dI}{dt}$$

$$\boxed{e = L \frac{dI}{dt}}$$

$$e = -L \frac{dI}{dt}$$

-ve sign opposite to direction of direction of flux.

$$L = \frac{e}{(dI/dt)}$$

Expression for mutual inductance:

$$e_M \propto \frac{dI_1}{dt}$$

$$e_M = -M \frac{dI_1}{dt}$$

$$M = \frac{e_M}{dI_1/dt}$$





Inductance in series



$$L_T = L_1 + L_2$$

Inductance in parallel

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$\text{or } L_T = \frac{L_1 + L_2}{L_1 L_2}$$

Energy stored in a magnetic field:

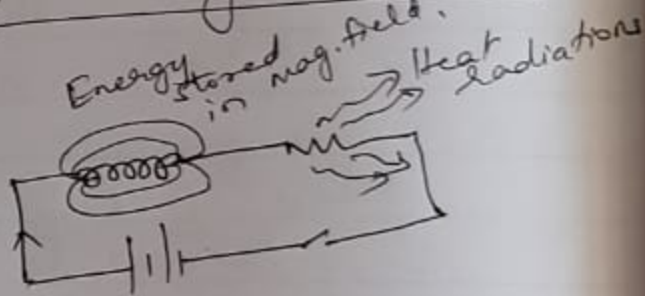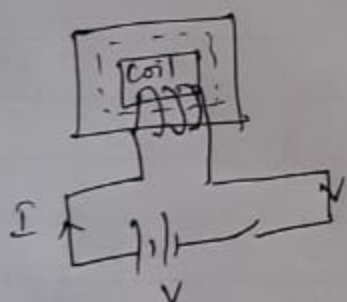

Energy supplied to the circuit is spent in two ways.

- 1) A part of supplied energy is spent to meet  $I^2 R$  losses and cannot be recovered.
- 2) The remaining part is spent to create magnetic flux around the coil and is stored in the magnetic field. When the field collapses, this stored energy is returned to the circuit.

### Instantaneous power:

(6)

$$p = e i = L i \frac{di}{dt}$$

Short interval of time  $dt$ , the energy due put into the magnetic field is equal to power multiplied by time  $dt$ .

$$dw = p dt = \left( L i \frac{di}{dt} \right) dt = L i di$$


$$W = \int_0^I L i di = \frac{1}{2} L I^2$$

Energy stored in magnetic field  $E = \frac{1}{2} L I^2$  joules

Magnetic energy stored  $= \frac{B^2}{2\mu_0}$  joules.
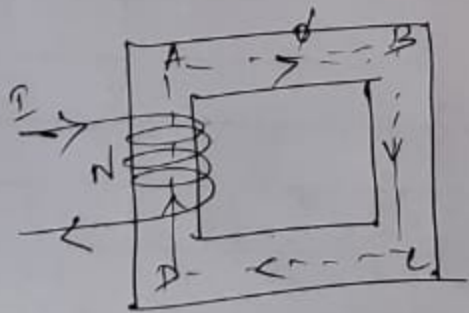
### Magnetic circuits:

The closed path followed by magnetic flux is called a magnetic circuit:



Consider a coil of  $N$  turns wound on an iron core. When a current  $I$  is passed through the coil magnetic flux  $\Phi$  is set up in the core.




Samsung Triple Camera  
Galaxy A30s

The flux follows a closed path <sup>(70)</sup> ABCDA. Hence ABCDA is the magnetic circuit.

m.m.f —  $NI$  ampere turns.  
magneto  
motive  
force

The magnetic circuit offers a resistance to the magnetic flux is called as reluctance of the magnetic circuit.

Series magnetic circuit:

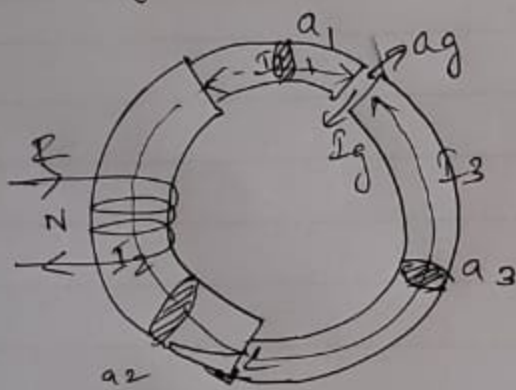

$$\text{Total reluctance} = \frac{l_1}{a_1 \mu_0 \mu_{r1}} + \frac{l_2}{a_2 \mu_0 \mu_{r2}} + \frac{l_3}{a_3 \mu_0 \mu_{r3}} + \frac{l_g}{a_g \mu_0}$$

Total m.m.f = Magnetic flux  $\times$  Total reluctance

$$\therefore \Phi = \frac{F}{R} = \frac{NI}{\frac{l_1}{a_1 \mu_0 \mu_{r1}} + \frac{l_2}{a_2 \mu_0 \mu_{r2}} + \frac{l_3}{a_3 \mu_0 \mu_{r3}} + \frac{l_g}{a_g \mu_0}}$$

$$= \frac{B_1}{\mu_0 \mu_{r1}} \times l_1 + \frac{B_2}{\mu_0 \mu_{r2}} \times l_2 + \frac{B_3}{\mu_0 \mu_{r3}} \times l_3 + \frac{B_g}{\mu_0} \times l_g$$



Samsung Triple Camera  
Galaxy A30s




8

$$= H_1 I_1 + H_2 I_2 + H_3 I_3 + H_g I_g.$$

where  $H = \frac{B}{\mu_0 \mu_r}$

### Parallel Magnetic Circuits:-

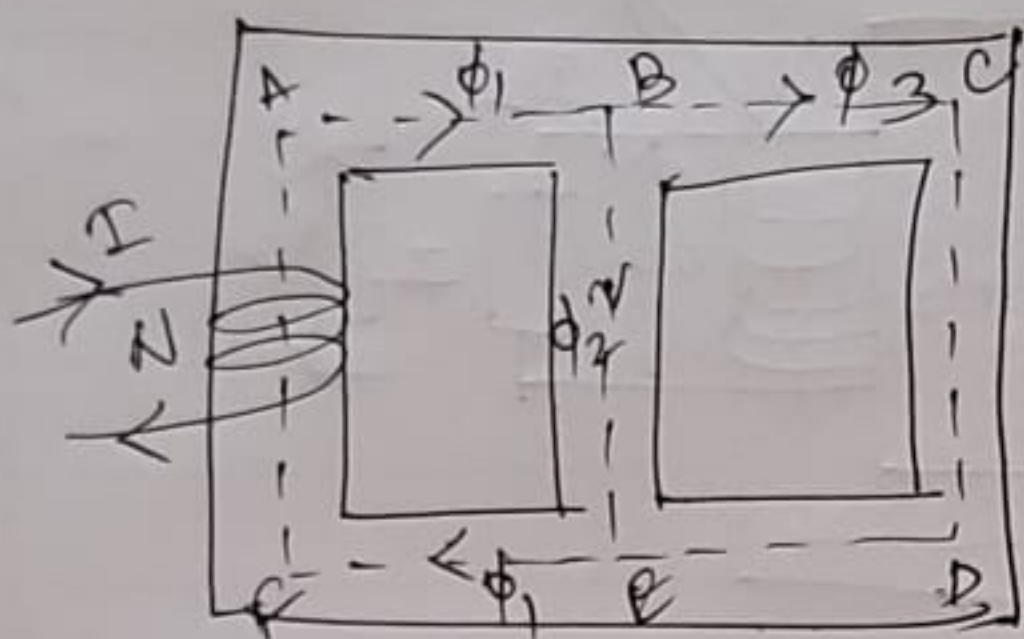

Here there are  $N$  turns, wound on a limb  $AF$  carries a current  $I$

A magnetic circuit which has more than one path for magnetic flux is called a parallel magnetic circuit.

The magnetic flux  $\Phi_1$  is divided into

two paths.

① magnetic flux  $\Phi_2$  passes along the path  $BE$

② magnetic flux  $\Phi_3$  follows the path  $BCDE$

clearly  $\Phi = \Phi_1 + \Phi_2$

The magnetic paths  $BE$  and  $BCDE$  are in parallel and form a parallel mag. circuit



The ampere-turns required for the (9), parallel circuit is equal to AT required for any one of the paths.

$S_1$  = reluctance of the path EFAB

$S_2$  = reluctance of the path BE

$S_3$  = reluctance of the path BCDE

Total mmf required = mmf of path EFAB  
+ mmf of path BE or BCDE

$$NI = \phi_1 S_1 + \phi_2 S_2$$

$$= \phi_1 S_1 + \phi_3 S_3$$

The reluctances  $S_1$ ,  $S_2$  and  $S_3$  must be determined from a calculation of  $\frac{l}{\mu_r \mu_0}$  for those paths of magnetic circuit in which  $\phi_1$ ,  $\phi_2$  and  $\phi_3$  exist respectively.




## Transformer:-

PAGE NO.

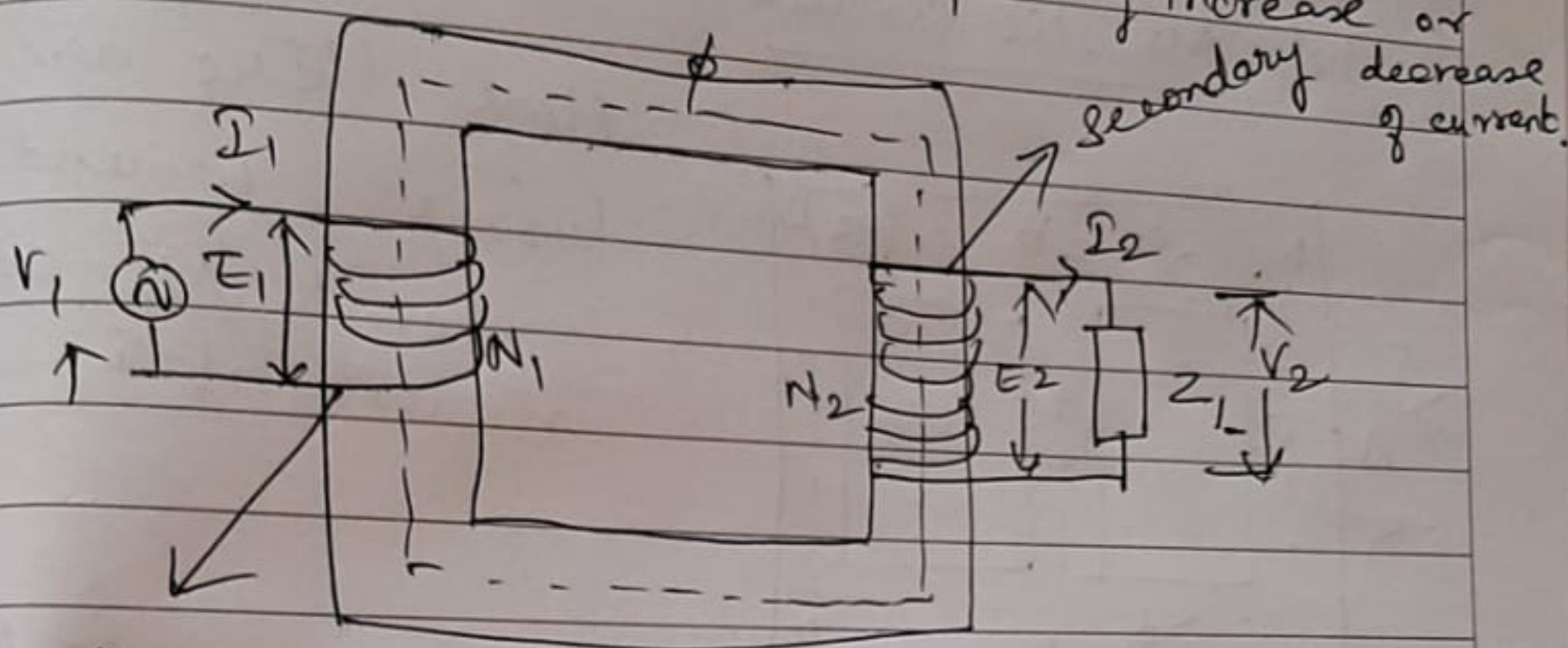10.

It is a static a.c. machine used for raising or lowering the voltage of an ac supply with a corresponding increase or decrease of current.



Primary  
Consists of two windings primary and secondary wound on a magnetic core. The winding connected to a.c source is called primary and the one connected to load is called secondary.

The alternating voltage whose magnitude is to be changed is applied to the primary. Depending upon the number of turns of the primary ( $N_1$ ) and secondary ( $N_2$ ) an alternating emf is induced in the secondary. The induced emf  $E_2$  appears across the load. If  $V_2 > V_1$ , it is called as step-up transformer. On the other hand if  $V_2 < V_1$ , it is called as step down transformer.



## Principle:

PAGE NO.

117

It is based on mutual inductance between two coils wound on the same laminated core.

## Working:-

When an alternating voltage is applied to the primary, an alternating flux  $\phi$  is set up in the core. The alternating flux links both the windings and induces emfs  $E_1$  in the primary and  $E_2$  in the secondary according to Faraday's law of electromagnetic induction.

$$E_1 = -N_1 \frac{d\phi}{dt}$$

$$E_2 = -N_2 \frac{d\phi}{dt}$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} \dots$$


If  $N_2 > N_1$ , then  $E_2 > E_1$  - step up transformer

If  $N_2 < N_1$ , then  $E_2 < E_1$  - step down transformer

Thus the transformer enables to transfer a.c power from one circuit to another with a change in voltage level.



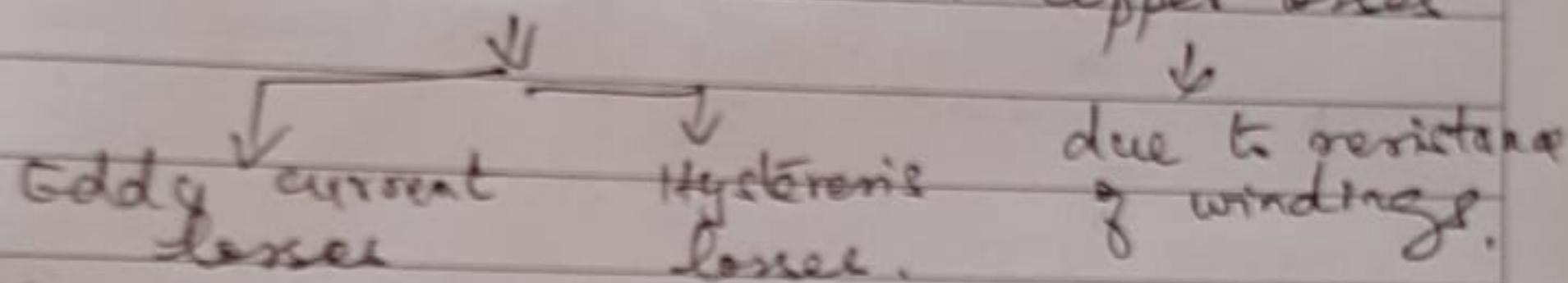- ① Based on em induction
- ② There is no electrical connection between primary and secondary. A.C power is transferred through magnetic flux from primary to secondary
- ③ There is no change in frequency between primary and secondary <sup>power</sup>
- ④ There are core losses and Copper losses



### Properties of an Ideal Transformer:

An ideal transformer has

- ① no losses due to winding resistance
- ② no leakage flux (same flux linked with both coils)
- ③ no Iron losses (eddy and hysteresis)


Though we cannot have an ideal transformer it helps us to analyse the practical transformer

Consider an ideal transformer on no load.

Secondary is open. The primary is simply a coil of pure inductance. When an a.c voltage is applied to the primary it draws a small magnetising current  $I_m$  which lags behind the applied voltage by  $90^\circ$ . The a.c current  $I_m$



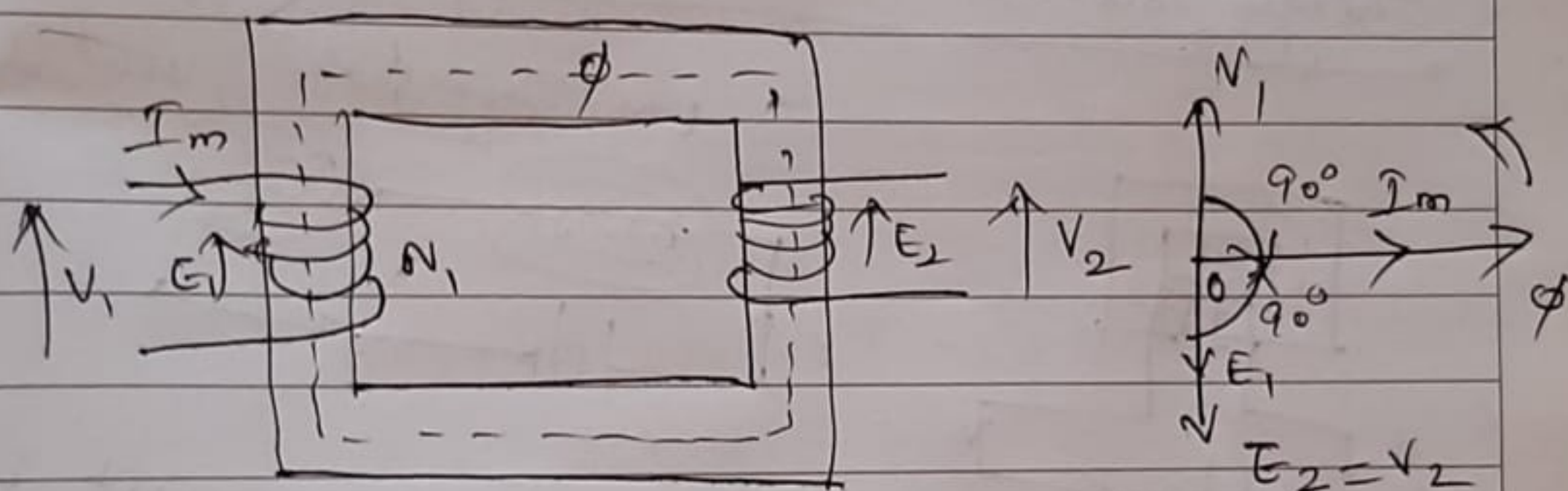produced an alternating flux  $\phi$ , which is proportional and in phase with  $I_m$ . The alternating flux links both the windings and induces an emf  $E_1$  in the primary and  $E_2$  in the secondary. The primary emf  $E_1$  is equal to  $V_1$ , but in opposite direction. Both  $E_1$  and  $E_2$  lag behind flux  $\phi$  by  $90^\circ$ . Magnitude depends upon no of turns.



Phasor diagram

$\phi$  is taken as reference since it is common to both the windings.

Consider alternating voltage  $V_1$  of frequency  $f$  is applied to the primary. The sinusoidal flux  $\phi$  produced by the primary

$$\phi = \phi_m \sin \omega t$$



Instantaneous emf produced in the primary is  $e_1$

$$e_1 = -N_1 \frac{d\phi}{dt} = -N_1 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= -\omega N_1 \phi_m \cos \omega t$$

$$= -2\pi f N_1 \phi_m \cos \omega t$$

$$= 2\pi f N_1 \phi_m \sin(\omega t - 90^\circ)$$

$$E_{m1} = 2\pi f N_1 \phi_m$$

The rms value of  $E_1$  of the primary emf is

$$E_1 = \frac{E_{m1}}{\sqrt{2}} = \frac{2\pi f N_1 \phi_m}{\sqrt{2}}$$

$$E_1 = 4.44 f N_1 \phi_m$$

$$E_2 = 4.44 f N_2 \phi_m$$

For an ideal transformer

$$E_1 = V_1 \text{ and } E_2 = V_2$$

$$\frac{E_1}{E_2} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$E_1$  and  $E_2$   
lag behind  $\phi$   
primary &c

$$\text{or } \frac{E_1}{N_1} = \frac{E_2}{N_2}$$

### ① Magnetic materials :-

Magnetic field :-

The force experienced by magnetic material, around which there exists a force which attracts magnetic material like iron filings.

### ② Magnetic force : (F)

$$F \propto \frac{m_1 m_2}{r^2}$$


$$F = k \frac{m_1 m_2}{r^2}$$

$$F = \frac{\mu_0 \mu_r}{4\pi} \frac{m_1 m_2}{r^2} \text{ N}$$
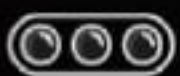
### ③ Magnetic moment (M)

$$M = m \times 2l$$

Product of the pole strength and length of the magnet. It is measured in  $\text{A/m}^2$ .





### ④ Permeability of the medium:

②

$$\mu = \mu_0 \times \mu_r$$

Absolute permeability of a medium or material is defined as the product of permeability of free space ( $\mu_0$ ) and the relative permeability of the medium.

$$\mu = \mu_0 \times \mu_r$$

### ⑤ Magnetic field Intensity: (H)

The space around the magnet in which its magnetic influence is felt. A magnetic field exists at a point, it can exert a force on the moving charge.

$$F = \frac{\mu_0 \mu_r}{4\pi} \times \frac{m \times l}{r^2} \text{ A/m}$$

### ⑥ Intensity of Magnetization: (I)

$$I = \frac{\text{magnetic moment (M)}}{\text{Volume (V)}} = \frac{M}{V}$$

$$I = \frac{M}{V} = \frac{m \times l}{a \times l} = \frac{m}{a} \text{ wb/m}^2$$

The measure of magnetization of a magnetized specimen is called intensity of magnetization.





② Relation Between susceptibility and permeability

$$\mu = \mu_0 \mu_r = B/H$$

When a magnetic material of cross-sectional area  $A$  and relative permeability  $\mu_r$  is placed in a uniform magnetic field  $H$ , two types of induction pass through it. one is due to magnetizing field  $H$  and the other due to the material itself being magnetised by induction. The total flux density  $B$  is

$$B = \mu_0 H + \mu_0 I$$

$$\mu = \mu_0 \mu_r = \frac{B}{H}$$

$$= \frac{\mu_0 H + \mu_0 I}{H}$$

$$\mu_0 \mu_r = \mu_0 + \frac{\mu_0 I}{H} = \mu_0 + \mu_0 \chi$$

Dividing both sides by  $\mu_0$

$$\mu_r = 1 + \chi$$



⑧ Magnetic susceptibility :  $\chi$

$$\chi = \frac{I}{H}$$

(4)

It measures the ease with which a specimen ~~measures~~ can be magnetised.

⑨ Magnetic flux density :

$$B = \frac{\phi}{A} \quad \text{weber/m}^2$$

It is the total number of lines of force per unit area due to magnetising field induced in the substance.

