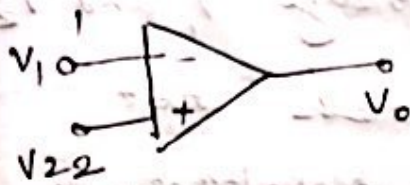


Op. Amplifier

(1)



Depending upon whether input is applied to 1 input or 2 inputs op-Amp can have two or one inputs. Similarly output is also either single or double ended.

It has minimum five terminals.

1. inverting input terminals
2. non-inverting input terminal.
3. output terminal
4. positive bias supply terminal.
5. negative bias supply terminal.

- sign - represents inverting terminals
+ sign - " non-inverting "

This means that a signal applied at negative input terminal will appear amplified but phase inverted at the output terminal. Similarly input signal applied to the positive terminal will appear amplified and inphase at the output.

The +ve and -ve sign indicates phase reversal not the voltage V_1 and V_2 .

Also + and - sign does not indicate that +ve input voltage to be connected to + or -ve input signal to -. It can be reversed.

Op-Amp characteristics :

1) Op-Amp is operated without connecting to any resistor or capacitor from its output to any one of the inputs, it is said to be in the open-loop condition. The word open loop means there is no feedback.

2) Its open loop gain is A_v is infinite
 $A_v = -\infty$

3) Its input resistance R_i is infinite
 $R_i = \infty \text{ ohm.}$

4) Its output resistance R_o is zero
 $R_o = 0 \Omega$

5) It has got infinite bandwidth i.e. it has flat frequency response from dc to infinity.

1) Infinite input resistance means the input current $i = 0$.

It is a voltage controlled device.


2) $R_o = 0$ means, V_o is not dependent on the load resistance connected across the output.

3) For an ideal op-Amp $A_v = \infty$ but actually it is very high. (10^6)

For input supply of $V_{cc} = \pm 15V$, $A_v = 10^6$, V_o can be limited to $15/10^6 = 15\mu V$

$1\mu V$ can become $1V$.

Op-Amp with Negative feedback:

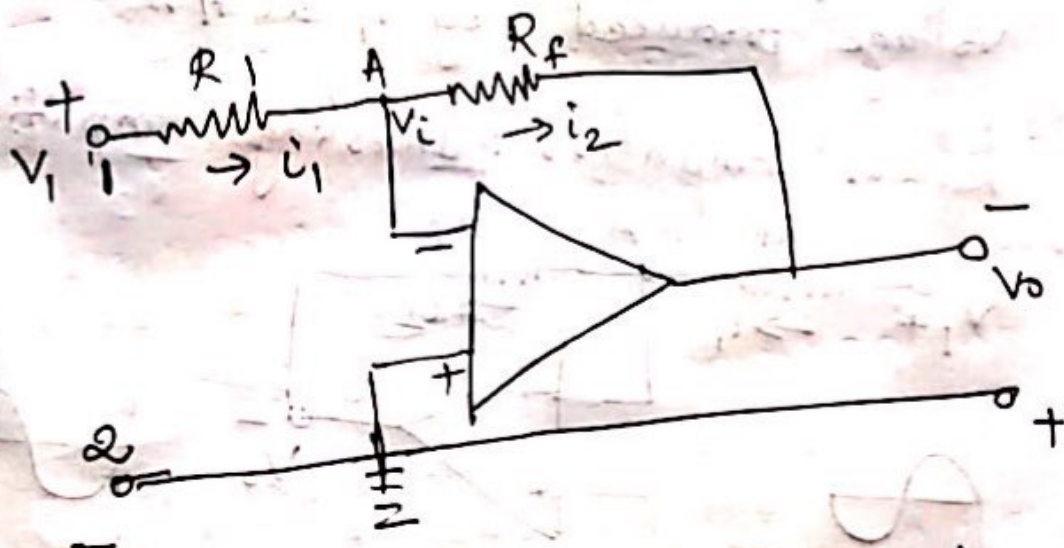

R_f - feed a portion of the o/p into the input. Since the input and feedback


currents are added at point A⁽⁴⁾. It is called as summing point.

When V_i is applied, point A attains some positive potential and at the same time V_o is brought into existence. Due to the negative feedback, some fraction of the V_o voltage is fed back to the point A antiphase with the voltage V_i .

The algebraic sum of the two voltages is almost zero $V_i \approx 0$.

Negative feed back voltage_A is exactly equal to the positive voltage produced by V_i at A.

Linear Amplifier: Inverting Amplifier

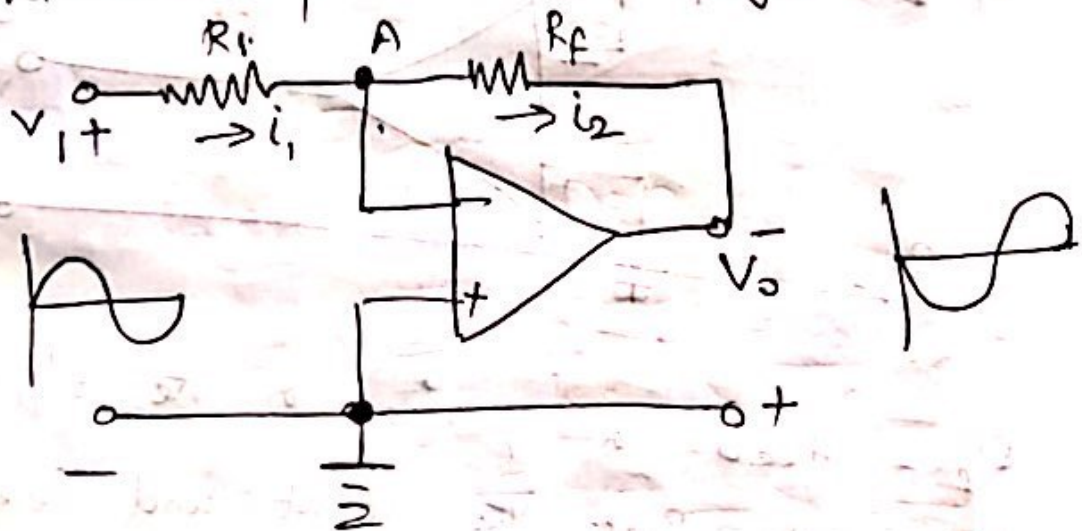

Gain $i_1 = \frac{V_{in}}{R_1} = \frac{V_1}{R_1}$

$i_2 = -\frac{V_o}{R_f}$

$i_1 - (-i_2) = 0 \quad ; \quad \frac{V_1}{R_1} + \frac{V_o}{R_f} = 0$

$\frac{V_o}{R_f} = -\frac{V_1}{R_1} \quad \text{or} \quad \frac{V_o}{V_1} = -\frac{R_f}{R_1}$


$A_v = -\frac{R_f}{R_1} \quad \text{or} \quad A_v = -K$
 Also $V_o = -K V_{in}$

K - constant

Voltage gain depends on R_1 and R_f - external resistors

Not on op amp parameters.

Non-inverting:

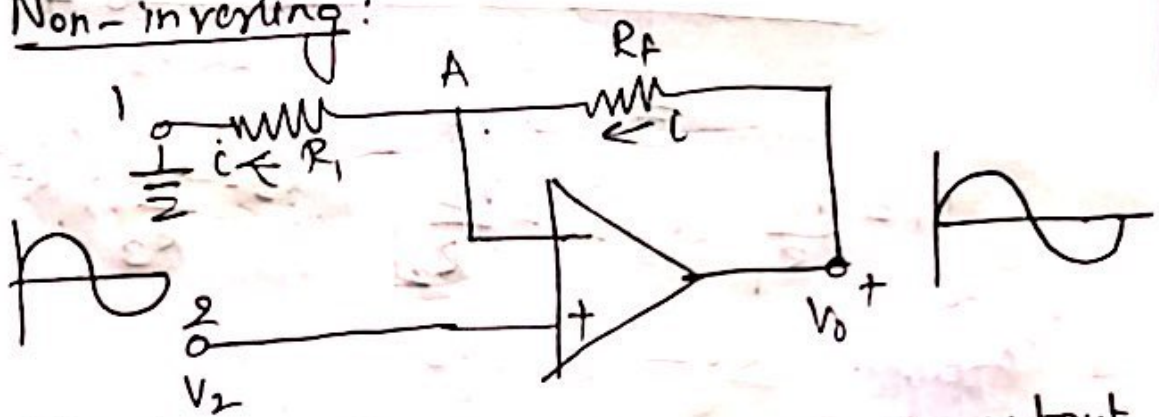

Negative feedback is given the output is multiplied by a positive scalar.
 → constant

Since V_2 is applied to non-inverting terminal called as non-inverting amplifier


V_0 and $V_2 = +ve$ (b)
Voltage across R_1 is the input voltage

$$V_{in} = V_2 = iR_1; \quad V_0 = i(R_1 + R_F)$$

$$A_v = \frac{V_0}{V_{in}} = \frac{i(R_1 + R_F)}{iR_1}$$

$$A_v = \frac{R_1 + R_F}{R_1} = 1 + \frac{R_F}{R_1}$$

Adder or Summer:

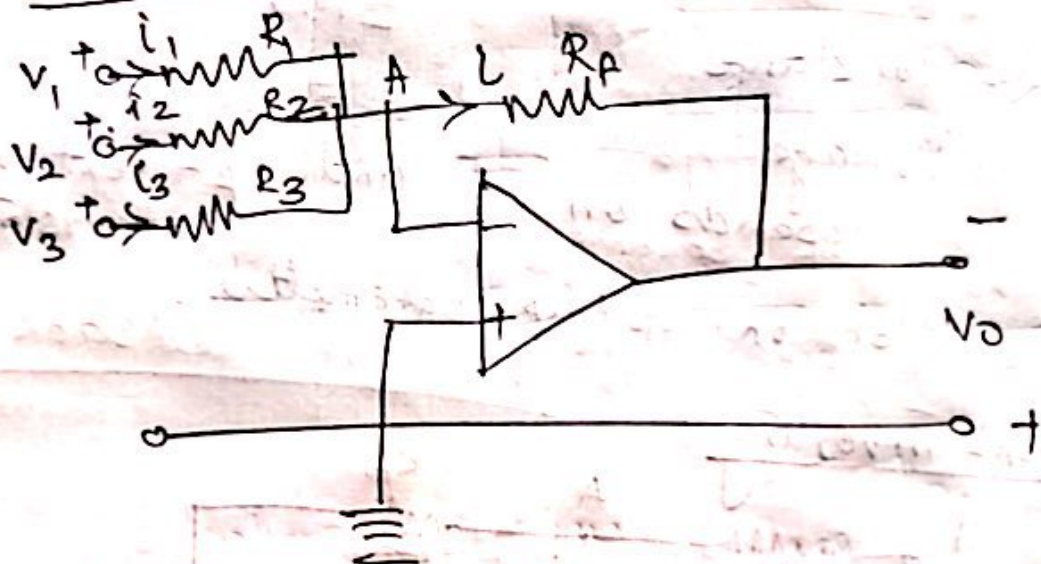

$$i_1 = \frac{V_1}{R_1}; \quad i_2 = \frac{V_2}{R_2}; \quad i_3 = \frac{V_3}{R_3}; \quad i = \frac{-V_0}{R_F}$$

Applying KCL

$$i_1 + i_2 + i_3 + (-i) = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} - \left(\frac{-V_0}{R_F} \right) = 0$$

$$V_0 = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$

$$V_o = -(k_1 V_1 + k_2 V_2 + k_3 V_3) \quad (7)$$

— sign - inverting the i/p terminal


$$R_1 = R_2 = R_3 = R$$

$$\therefore V_o = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

$$= -k (V_1 + V_2 + V_3)$$

Algebraic sum of the input voltages.

Subtractor:

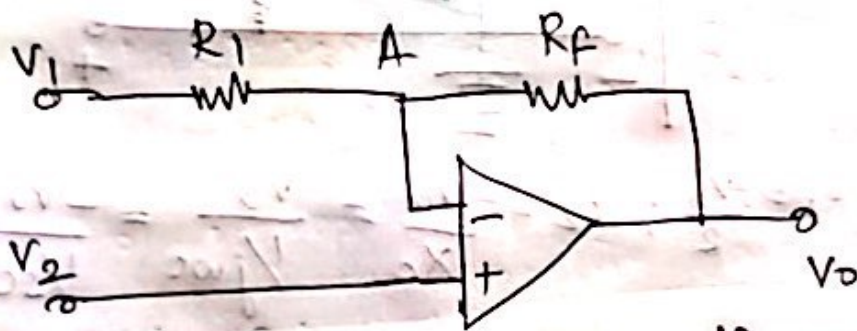

Applying super position theorem.

$$V_o = V_o' + V_o''$$

↓
o/p produced by V_1

↓
o/p produced by V_2

$$V_o' = -\frac{R_f}{R_1} V_1 \quad ; \quad V_o'' = \left(1 + \frac{R_f}{R_1}\right) V_2$$

$$\therefore V_o = \left(1 + \frac{R_f}{R_1}\right) V_2 - \frac{R_f}{R_1} V_1$$


$$R_F = R_1 \text{ and } R_F/R_1 = 1 \quad (6)$$

$$V_o = \frac{R_F}{R_1} (V_2 - V_1) = k(V_2 - V_1)$$

$$\text{If } R_F = R_1$$

$$V_o = (V_2 - V_1) \text{ - diff of two } 1\text{p} \text{ voltages.}$$

Integrator

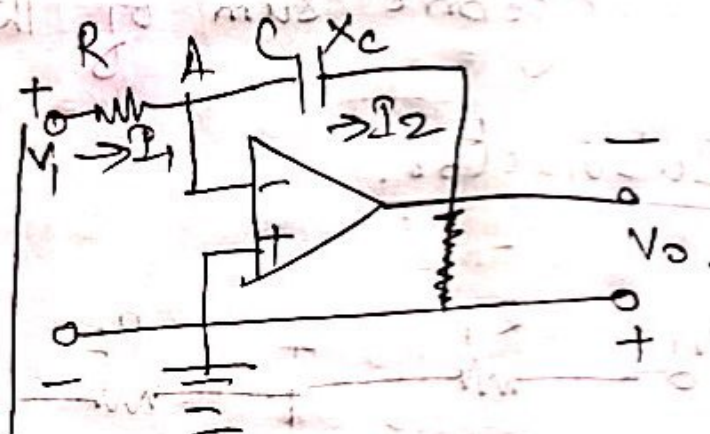

$$i_1 = \frac{V_1}{R}; \quad i_2 = -\frac{V_o}{X_c} = \frac{V_o}{1/j\omega C} = -\frac{V_o}{1/sC}$$

$$\text{where } s = j\omega \text{ Laplace notation}$$

$$i_1 = i_2$$

$$\frac{V_1}{R} = -sC V_o$$


$$\frac{V_o}{V_{in}} = \frac{V_o}{V_1} = -\frac{1}{sCR}$$

$$A_v = -\frac{1}{sCR}$$

$$V_o(t) = -\frac{1}{RC} \int V_1(t) dt$$

Differentiator:

(9)

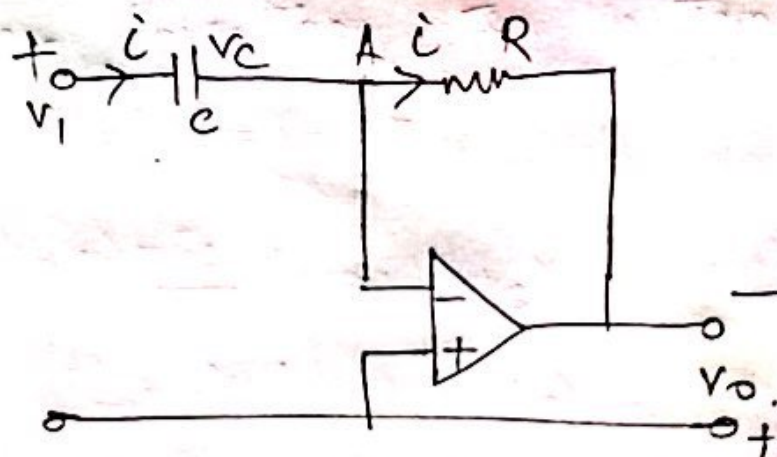

Differentiator circuit can be obtained by interchanging the resistor and capacitor of the integrator circuit.

$$i = \text{rate of change of charge} = \frac{dq}{dt}$$

$$q = CV_c$$

$$i = \frac{d}{dt} (CV_c) = C \frac{dV_c}{dt}$$

A - virtual ground.

$$V_o = -iR = -\left[C \cdot \frac{dV_c}{dt}\right] R$$

$$V_o = -iR = -CR \frac{dV_c}{dt}$$

V_o is proportional to the derivative of the input voltage. $-CR$ is constant.