


Magnitude Comparator

- It is a combinational circuit that compares two numbers and determines their relative magnitude.
- Consider the two numbers as A & B.
- Hence, it consists of three outputs that indicates:
 - $A > B$
 - $A = B$
 - $A < B$
- The circuit for comparing two n -bit numbers has 2^{2n} entries in the truth table and becomes too cumbersome.
- A comparator circuit possesses a certain amount of regularity.
- Digital functions that possess an inherent well-defined regularity can usually be designed by means of an algorithm
 - a procedure which specifies a finite set of steps that, if followed, give the solution to a problem.

Magnitude Comparator

- Consider two numbers, A(A_0) and B(B_0) with a single bit each.

Block Diagram:

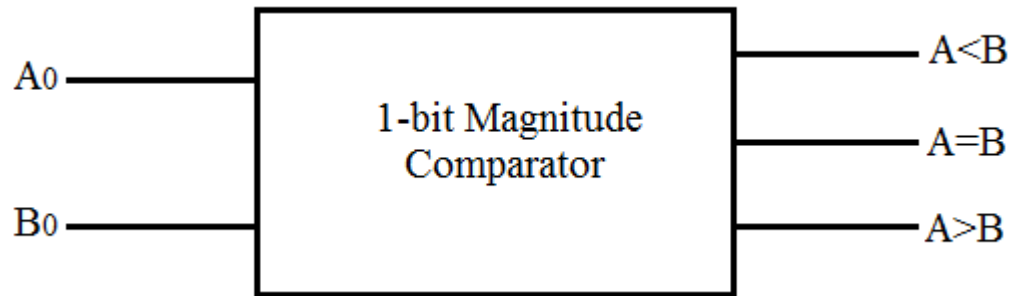

Truth Table:

A_0	B_0	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0


Functions:

$$(A < B) = A_0' B_0$$

$$(A > B) = A_0 B_0'$$

$$(A = B) = A_0' B_0' + A_0 B_0$$
$$= (A_0' B_0 + A_0 B_0)'$$

Circuit Diagram:

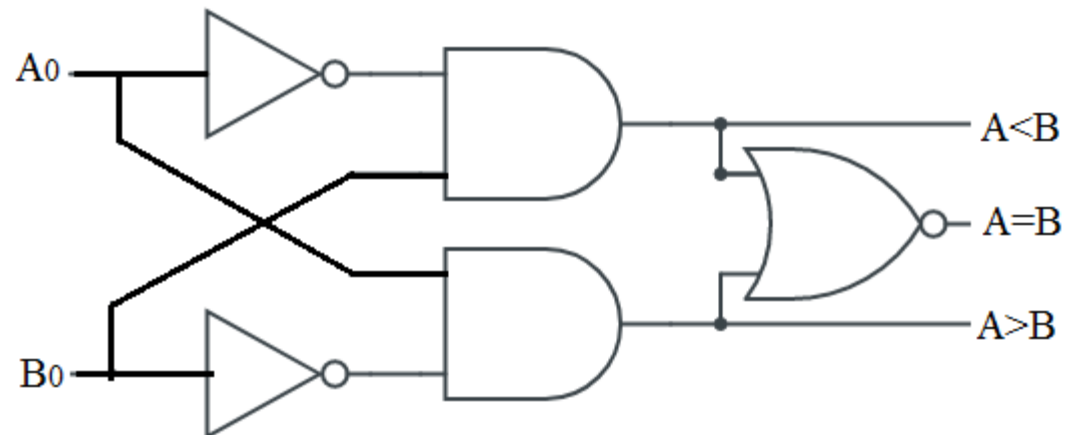

Magnitude Comparator

- Consider two numbers, A and B , with four digits each (Write the coefficients of the numbers in descending order of significance)

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

- $A=B$

- The two numbers are equal if all pairs of significant digits are equal:
 - $A_3 = B_3, A_2 = B_2, A_1 = B_1, \text{ and } A_0 = B_0.$
- When the numbers are binary, the digits are either 1 or 0, and the equality of each pair of bits can be expressed logically with an exclusive-NOR function as:

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3$$

- For equality to exist, all x_i variables must be equal to 1, a condition that dictates an AND operation of all variables:

$$(A = B) = x_3 x_2 x_1 x_0$$

- The binary variable $(A = B)$ is equal to 1 only if all pairs of digits of the two numbers are equal

Magnitude Comparator

- A>B and A<B


- we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position.
- If the two digits of a pair are equal, we compare the next lower significant pair of digits.
- The comparison continues until a pair of unequal digits is reached.
 - If the corresponding digit of A is 1 and that of B is 0, we conclude that A>B.
 - If the corresponding digit of A is 0 and that of B is 1, we have A<B.
- The sequential comparison can be expressed logically by the two Boolean

fun

$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$


$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

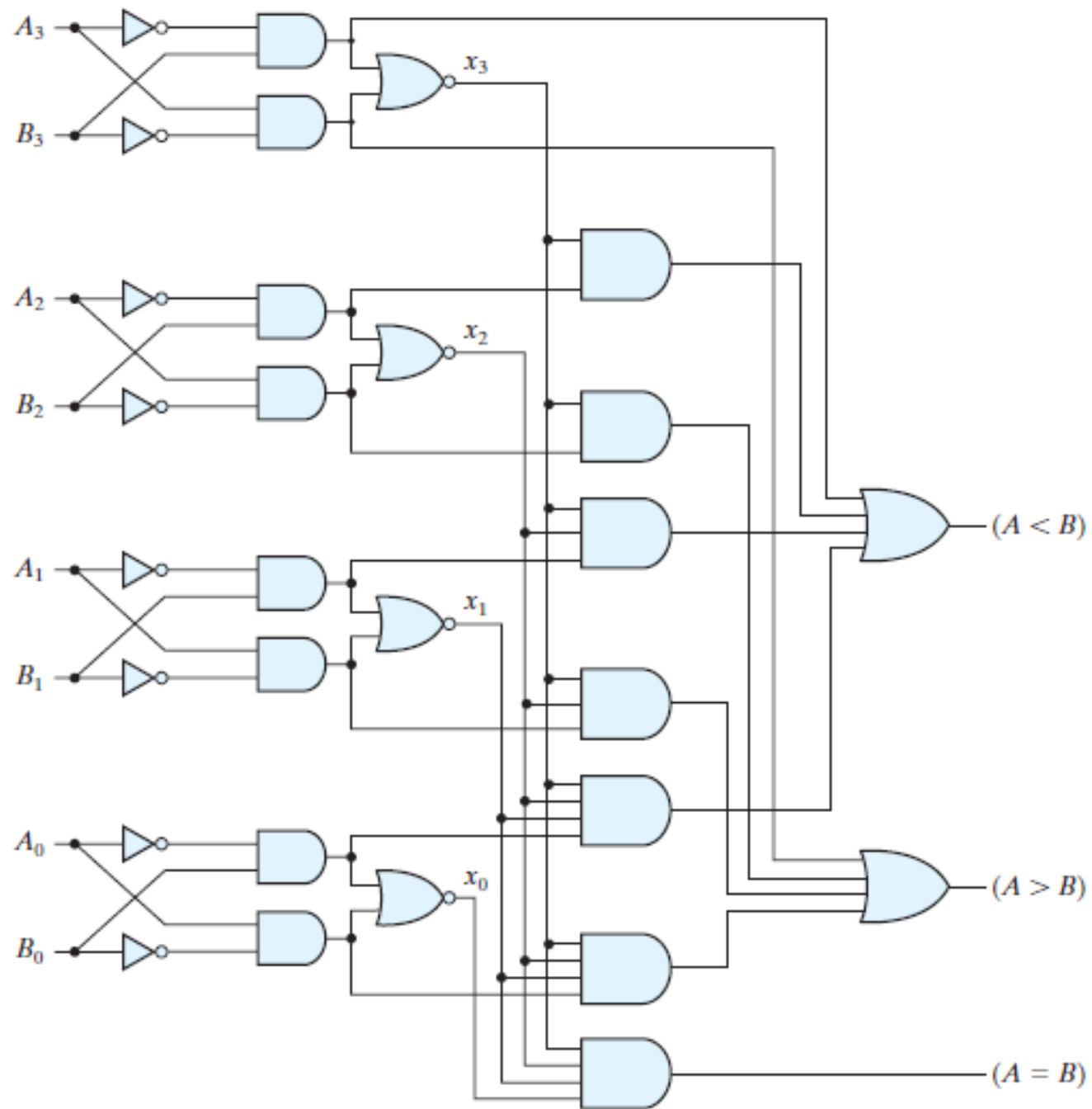- The symbols (A>B) and (A<B) are binary output variables that are equal to 1 when A>B and A<B, respectively.



Decoder

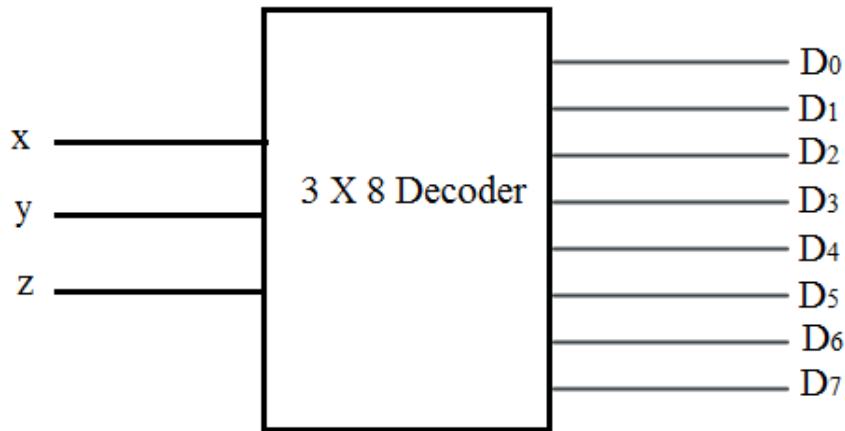- A decoder is a combinational circuit that converts binary information from n input lines to the maximum 2^n unique outputs
- If the decoder consists of three inputs the maximum number of output lines is eight.
- Block Diagram:




- Truth Table:

x	y	z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Decoder

- Circuit Diagram:

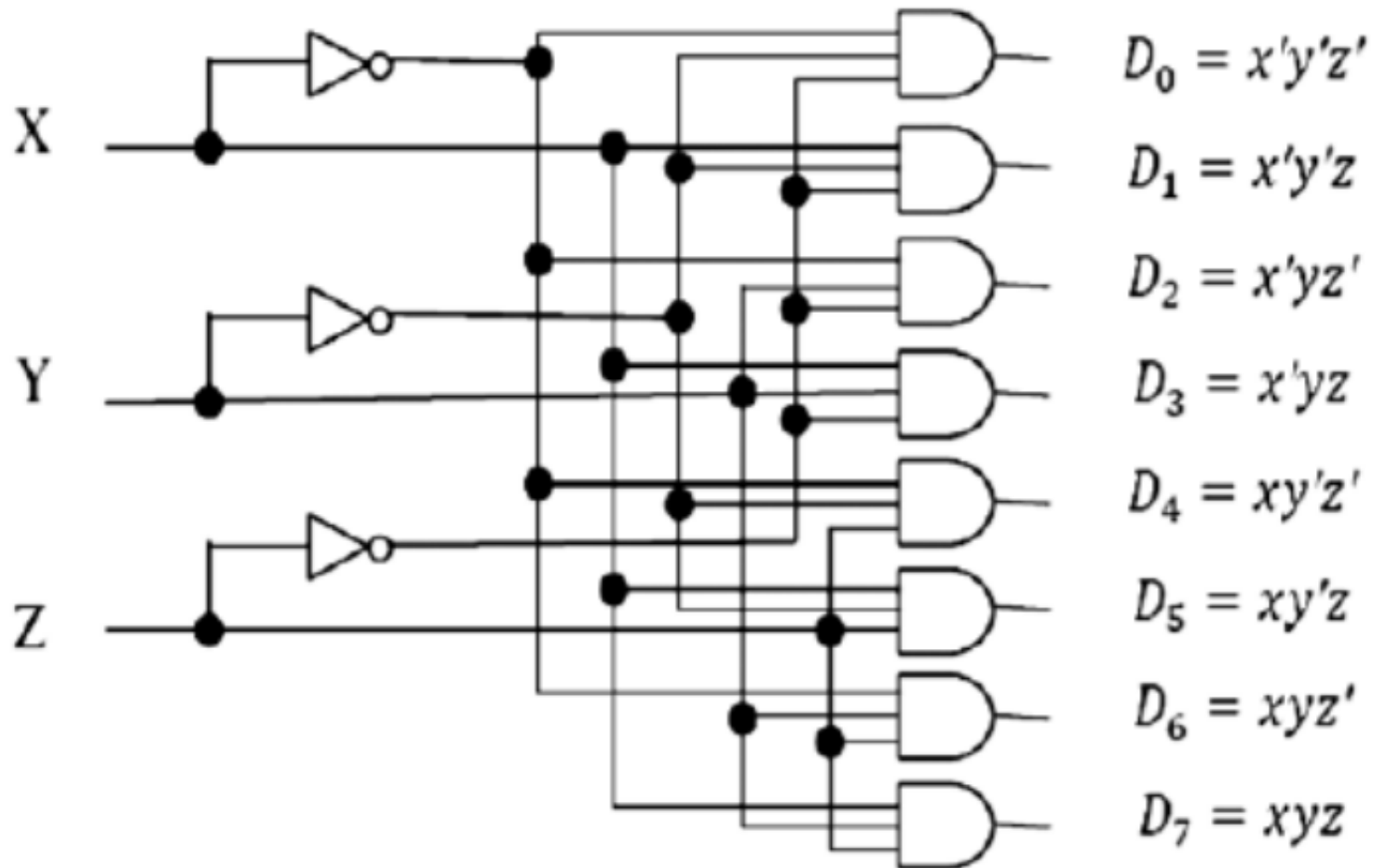

Decoder


- Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n line decoder and m OR gates.
 - For this the Boolean functions for the circuit must be expressed in sum of minterms form
 - Decoder is chosen that generates all the minterms of the n input variables
 - The inputs to each OR gate are selected from the decoder outputs according to the minterm list in each function.

Decoder

- Implement a full adder circuit with a decoder.

– Truth table:

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

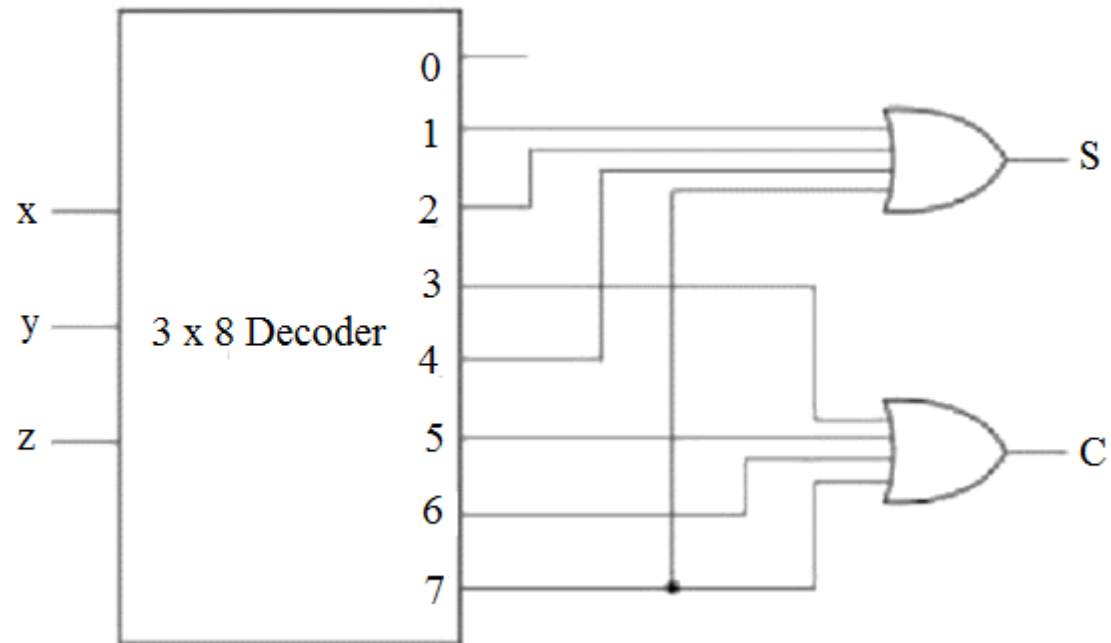

– Minterms form:

- $S(x,y,z) = \sum(1,2,4,7)$
- $C(x,y,z) = \sum(3,5,6,7)$

Active-Low Decoder

[illegible]